

## Chapter 2

### AC to DC Converters (Rectifiers)

#### 2.1 Introduction

A rectifier is a power electronic device that converts alternating current (AC) which periodically reverses direction, to direct current (DC) which flows in only one direction. The rectifiers can be classified as shown in Figure 2.1.

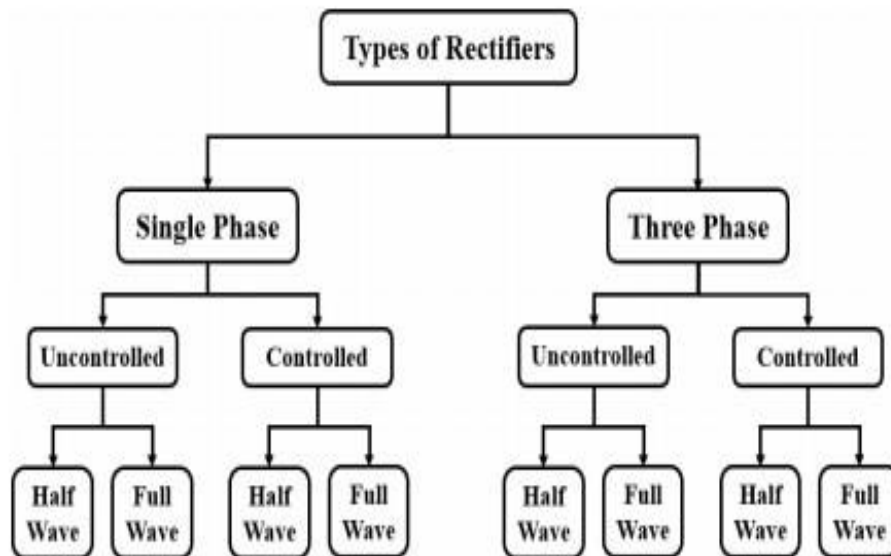


Figure 2.1: Classification of rectifiers.

## 2.2 Single-Phase Half-Wave Uncontrolled Rectifier

### 2.2.1 Case of Resistive Load

A basic single-phase half-wave uncontrolled rectifier with a resistive load is shown in Figure 2.2. For the positive half-cycle of the source in this circuit, the diode is ON

(forward biased). For the negative half-cycle of the source, the diode is reverse-biased, making the current zero. The voltage across the diode is the source voltage.

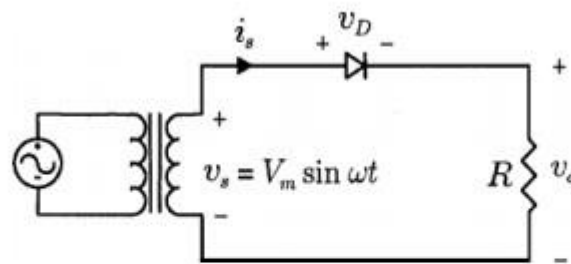


Figure 2.2: A single-phase half-wave uncontrolled rectifier with a resistive load.

Assuming that the transformer provides ideal sinusoidal voltage on its secondary winding, the voltage and current waveforms on resistive load and the voltage waveform on the diode are shown in Figure 2.3.

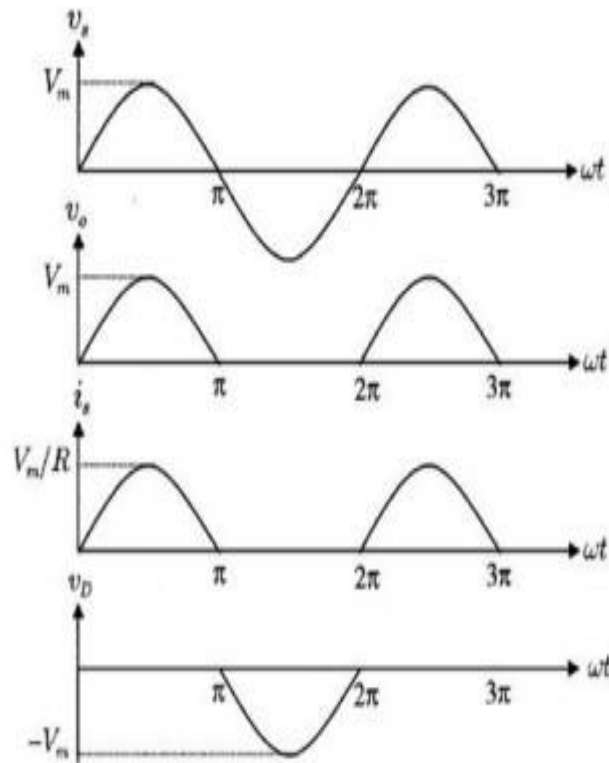


Figure 2.3: The waveforms of the single-phase half-wave uncontrolled rectifier with a resistive load.

The average (mean) value of output

$$\text{voltage, } V_{DC(Load)} = \frac{\text{Area}}{T} = \frac{1}{2\pi} \int_0^{\pi} v_m \sin \omega t d\omega t$$

$$V_{DC(Load)} = \frac{1}{2\pi} \int_0^{\pi} v_m \sin \omega t d\omega t$$

To make the solution simpler, we assume  $\omega t = \theta$

$$V_{DC(Load)} = \frac{1}{2\pi} \int_0^{\pi} v_m \sin \theta d\theta = \frac{v_m}{2\pi} [-\cos \theta]_0^{\pi} = -\frac{v_m}{2\pi} [\cos(\pi) - \cos(0)]$$

$$V_{DC(Load)} = \frac{v_m}{\pi}$$

The average value of output current,  $I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$

$$I_{DC(Load)} = \frac{v_m}{\pi R}$$

The RMS value of output voltage,  $V_{RMS(Load)} = \sqrt{\frac{1}{2\pi} \int_0^\pi [v_m \sin\theta]^2 d\theta}$

$$V_{RMS(Load)} = \sqrt{\frac{1}{2\pi} \int_0^\pi (v_m)^2 (\sin\theta)^2 d\theta} = \sqrt{\frac{(v_m)^2}{2\pi} \int_0^\pi \frac{1}{2} (1 - \cos 2\theta) d\theta}$$

$$V_{RMS(Load)} = \frac{v_m}{2\sqrt{\pi}} \sqrt{\int_0^\pi 1 d\theta - \int_0^\pi \cos 2\theta d\theta} = \frac{v_m}{2\sqrt{\pi}} \sqrt{[\theta]_0^\pi - [\sin 2\theta]_0^\pi}$$

$$V_{RMS(Load)} = \frac{v_m}{2\sqrt{\pi}} \sqrt{\pi}$$

$$V_{RMS(Load)} = \frac{v_m}{2}$$

The RMS value of output current,  $I_{RMS(Load)} = \frac{V_{RMS(Load)}}{R}$

$$I_{RMS(Load)} = \frac{v_m}{2R}$$

The average output DC power,  $P_{DC(load)} = V_{DC(load)} I_{DC(load)}$

The power delivered to resistive load,  $P_{AC(load)} = V_{AC(load)} I_{AC(load)}$

The input power factor,  $PF = \frac{P_{AC(load)}}{V_{s,RMS} I_{s,RMS}}$

The efficiency of a rectifier,  $\eta = \frac{P_{DC(load)}}{V_{s,RMS} I_{s,RMS}} * 100\%$

Lecture 2

**Example 1:** For the shown half-wave rectifier, the voltage source is a 120 V with a frequency of 60 Hz. The load resistor is 5  $\Omega$ . Determine:

- (a) The average load current.
- (b) The dc and ac power absorbed by the load.
- (c) The input power factor of the circuit.
- (d) The efficiency of the rectifier.

**(e) Solution:**

$$V_{s,RMS} = 120 \text{ V}, F = 60 \text{ Hz}, R = 5\Omega$$

(a)

$$I_{DC(Load)} = \frac{v_m}{\pi R} \quad v_m = \sqrt{2}V_{s,RMS}$$

$$I_{DC(Load)} = \frac{120\sqrt{2}}{5\pi} = 10.8 \text{ A}$$

$$(b) P_{DC(load)} = V_{DC(load)} I_{DC(load)} \quad , \quad V_{DC(load)} = \frac{v_m}{\pi} = \frac{120\sqrt{2}}{\pi} = 54 \text{ V}$$

$$P_{DC(load)} = (54)(10.8) = 583.2 \text{ Watt}$$

$$P_{AC(load)} = V_{AC(load)} I_{AC(load)} \quad , \quad V_{RMS(load)} = \frac{v_m}{2} = \frac{120\sqrt{2}}{2} = 84.9 \text{ V}$$

$$, \quad I_{RMS(load)} = \frac{V_{RMS}}{R} = \frac{84.9}{5} = 17 \text{ A}$$

$$P_{AC(load)} = (84.9)(17) = 1443.3 \text{ Watt}$$

$$(c) PF = \frac{P_{AC(load)}}{V_{s,RMS} I_{s,RMS}} = \frac{1443.3}{(120)(17)} = 0.707$$

$$(d) \eta = \frac{P_{DC(load)}}{V_{s,RMS} I_{s,RMS}} * 100\% = \frac{583.2}{(120)(17)} * 100\% = 28.5\%$$

### 2.2.2 Case of R-L Load

Industrial loads typically contain inductance as well as resistance. A basic single-phase half-wave uncontrolled rectifier with resistive and inductance load is shown in Figure 2.4.

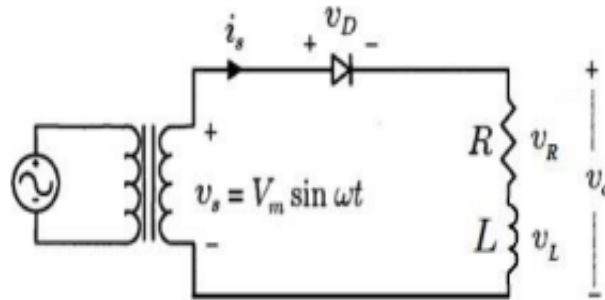


Figure 2.4: A single-phase half-wave uncontrolled rectifier with R-L load.

The Kirchhoff voltage law equation that describes the current in the circuit for the forward-biased ideal diode is:

$$v_m \sin(\omega t) = Ri(t) + L \frac{di(t)}{dt} \quad (1)$$

The solution of equation (1) can be obtained by expressing the current as the sum of the forced response and the natural response:

$$i(t) = i_f(t) + i_n(t)$$

The forced response for this circuit is the current that exists after the natural response has decayed to zero. In this case, the forced response is the steady-state sinusoidal current that would exist in the circuit if the diode was not present. This steady-state current can be found from phasor analysis, resulting in

$$i_f(t) = \frac{v_m}{Z} \sin(\omega t - \varphi)$$

The natural response is the transient that occurs when the load is energized. It is the solution to the homogeneous differential equation for the circuit without the source or diode.

$$\begin{aligned} i_n(t) \\ = A e^{-\frac{t}{\tau}} \end{aligned}$$

The final current equation can be written as:

$$i(\omega t) = \begin{cases} \frac{v_m}{Z} \left[ \sin(\omega t - \varphi) + \sin(\varphi) e^{-\frac{\omega t}{\tau}} \right], & 0 \leq \omega t \leq \beta \\ 0, & \beta \leq \omega t \leq 2\pi \end{cases}$$

$$\text{Where } Z = \sqrt{R^2 + (\omega L)^2}, \quad \varphi = \tan^{-1} \left( \frac{\omega L}{R} \right), \quad \tau = \frac{L}{R}$$

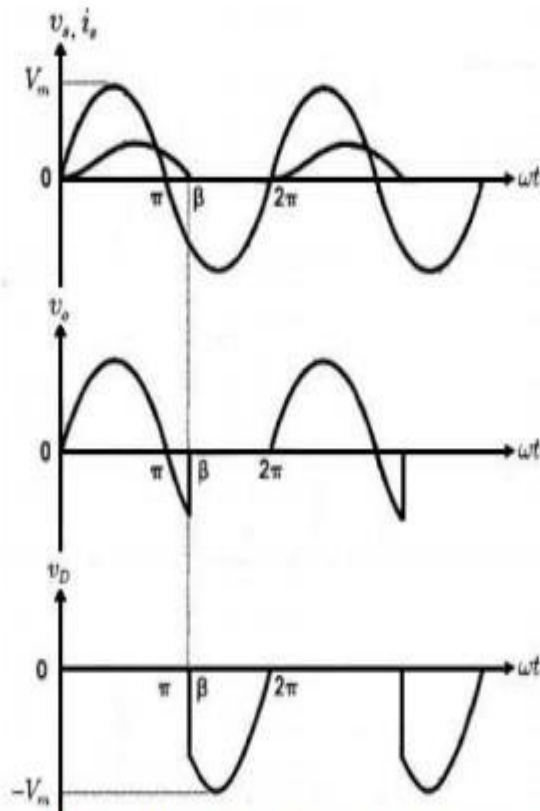


Figure 2.5: The waveforms of the single-phase half-wave uncontrolled rectifier with R-L load.

$\beta$  : The conduction angle of the diode

$$V_{DC(Load)} = \frac{1}{2\pi} \int_0^{\beta} v_m \sin \omega t d\omega t$$

$$V_{DC(Load)} = \frac{v_m}{2\pi} [1 - \cos(\beta)]$$

The average value of output current,  $I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$

$$I_{DC(Load)} = \frac{v_m}{2\pi R} [1 - \cos(\beta)]$$



The RMS value of output voltage,  $V_{RMS(Load)} = \sqrt{\frac{1}{2\pi} \int_0^\beta [v_m \sin(\omega t)]^2 d\omega t}$

$$V_{RMS(Load)} = \sqrt{\frac{v_m^2}{4\pi} \left[ \beta - \frac{1}{2} \sin(2\beta) \right]}$$

The RMS value of output current,  $I_{RMS(Load)} = \sqrt{\frac{1}{2\pi} \int_0^\beta [i(\omega t)]^2 d\omega t}$

**Example 2:** For the half-wave uncontrolled rectifier with R-L load, the voltage source is a 70.7 V with a frequency of 60 Hz. The load comprise resistance of 100  $\Omega$  and inductance of 0.1 H. Assume the conduction angle equal to 3.5 rad and then determine:

- An expression for the current in this circuit.
- The average current and voltage.
- The rms voltage.
- The efficiency of the rectifier if the RMS current is equal to 0.47 A.

**Solution:**

$$V_{s,RMS} = 70.7 V, \quad V_m = 100 V,$$

$$F = 60 Hz, \quad \omega = 377 rad/sec,$$

$$R = 100 \Omega, \quad L = 0.1H, \quad \beta = 3.5 rad = 201^\circ$$

(a)

$$i(\omega t) = \begin{cases} \frac{v_m}{Z} \left[ \sin(\omega t - \varphi) + \sin(\varphi) e^{-\frac{\omega t}{\tau}} \right], & 0 \leq \omega t \leq \beta \\ 0 & , \beta \leq \omega t \leq 2\pi \end{cases}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \sqrt{(100)^2 + (37.7)^2} = 106.9\Omega$$

$$\varphi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \tan^{-1} \left( \frac{37.7}{100} \right) = 20.7$$

$$\tau = \frac{L}{R} = \frac{0.1}{100} = 0.001$$

$$i(\omega t) = \begin{cases} 0.936 \left[ \sin(\omega t - 20.7) + \sin(20.7) e^{-\frac{\omega t}{0.377}} \right], & 0 \leq \omega t \leq \beta \\ 0 & , \beta \leq \omega t \leq 2\pi \end{cases}$$

$$(b) I_{DC(Load)} = \frac{v_m}{2\pi R} [1 - \cos(\beta)]$$

$$I_{DC(Load)} = \frac{100}{2\pi(100)} [1 - \cos(201)] = 0.308A$$

$$V_{DC(Load)} = \frac{v_m}{2\pi} [1 - \cos(\beta)]$$

$$V_{DC(Load)} = \frac{100}{2\pi} [1 - \cos(201)] = 30.8V$$

(c)

$$V_{RMS(Load)} = \sqrt{\frac{v_m^2}{4\pi} \left[ \beta - \frac{1}{2} \sin(2\beta) \right]}$$

$$V_{RMS(Load)} = \sqrt{\frac{100^2}{4\pi} \left[ 3.5 - \frac{1}{2} \sin(2(201)) \right]} = 50.2V$$

$$(e) \eta = \frac{P_{DC(load)}}{V_{s,RMS} I_{s,RMS}} * 100\% = \frac{V_{DC(load)} I_{DC(load)}}{V_{s,RMS} I_{s,RMS}} * 100\%$$

### 2.2.3 Case of R-L Load with Freewheeling Diode

A freewheeling diode can be connected across an R-L load as shown in Figure 2.6 (a). The freewheeling diode is used to prevent the output voltage from becoming negative. In addition, the energy stored in inductance is transferred to resistance load through the freewheeling diode, which means the system efficiency is improved.

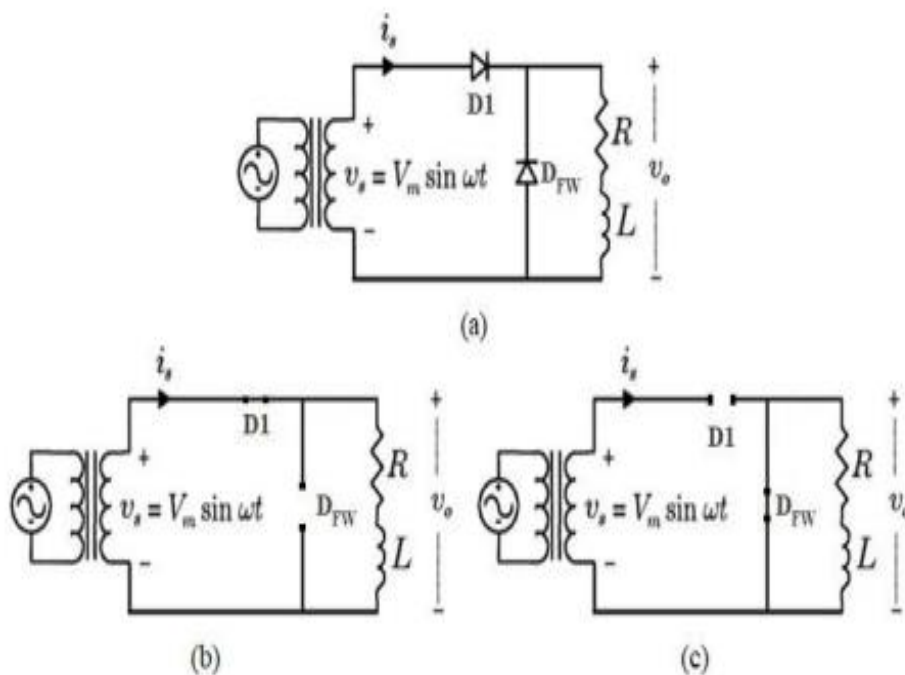


Figure 2.6: A single-phase half-wave uncontrolled rectifier with R-L load using freewheeling diode.

For a positive half-cycle of the source:

- D1 is on.
- D<sub>FW</sub> is off.
- The equivalent circuit is the same as that of Figure 2.6 (b).

- The voltage across the R-L load is the same as the source.

For a negative half-cycle of the source:

- $D_1$  is off.
- $D_{FW}$  is on.
- The equivalent circuit is the same as that of Figure 2.6 (c).
- The voltage across the R-L load is zero.

### 23 Single-Phase Full-Wave Bridge Uncontrolled Rectifier

A basic single-phase full-wave bridge uncontrolled rectifier with a resistive load is shown in Figure 2.7. This type of single-phase rectifier uses four individual rectifying diodes connected in a closed loop “bridge” configuration to produce the desired output. The four diodes labelled  $D_1$  to  $D_4$  are arranged in “series pairs” with only two diodes conducting current during each half cycle. The voltage and current waveforms on resistive load and the voltage waveform on the diodes are shown in Figure 2.8.

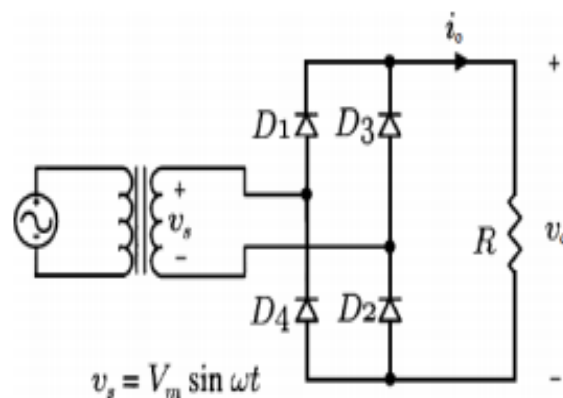


Figure 2.7: A single-phase full-wave bridge uncontrolled rectifier with a resistive load.

During the positive half cycle of the supply, diodes  $D_1$  and  $D_2$  conduct in series while diodes  $D_3$  and  $D_4$  are reverse biased and the current flows through the load.

- During the negative half cycle of the supply, diodes  $D_3$  and  $D_4$  conduct in series, but diodes  $D_1$  and  $D_2$  switch “OFF” as they are now reverse biased. The current flowing through the load is the same direction as before.


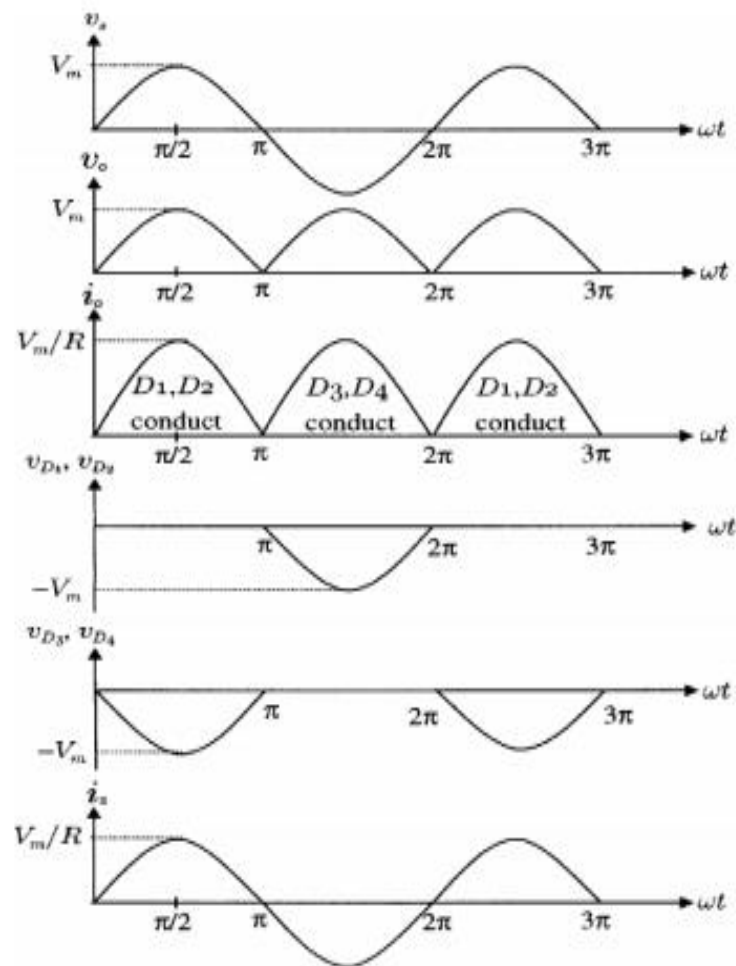


Figure 2.8: The waveforms of the single-phase full-wave bridge uncontrolled rectifier with a resistive load.

Lecture: 2

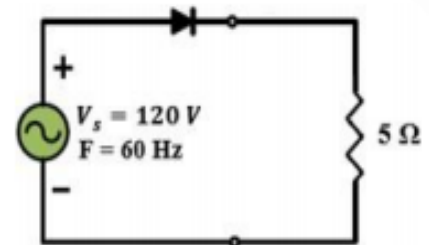

$$V_{DC(\text{Load})} = \frac{1}{\pi} \int_0^{\pi} v_m \sin \omega t d\omega t$$

$$V_{DC(\text{Load})} = \frac{2v_m}{\pi}$$

$$I_{DC(\text{Load})} = \frac{V_{DC(\text{Load})}}{R}$$

$$I_{DC(\text{Load})} = \frac{2v_m}{\pi R}$$

$$V_{RMS(\text{Load})} = \sqrt{\frac{1}{\pi} \int_0^{\pi} [v_m \sin \omega t]^2 d\omega t}$$

$$V_{RMS(\text{Load})} = \frac{v_m}{\sqrt{2}}$$

$$I_{RMS(\text{Load})} = \frac{V_{RMS(\text{Load})}}{R}$$

$$I_{RMS(\text{Load})} = \frac{v_m}{\sqrt{2}R}$$

Peak repetitive diode current,  $I_m = \frac{v_m}{R}$

$$I_{DC(\text{diode})} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t d\omega t = \frac{I_m}{\pi}$$

$$I_{RMS(\text{diode})} = \frac{1}{2\pi} \int_0^{\pi} [I_m \sin \omega t]^2 d\omega t = \frac{I_m}{2}$$

**Example 3:** The single-phase full-wave bridge uncontrolled rectifier is supported by a 120 V source. If the load resistance is 10.8  $\Omega$ , find:

Lecture: 2

- a) The DC voltage across the load
- b) The DC load current.
- c) The average current in each diode.
- d) The DC output power.
- e) The rectifier efficiency.
- f) The ripple factor.

**Solution:**

$$V_{s,RMS} = 120 V, \quad R = 10.8 \Omega$$

(a)

$$V_{DC(Load)} = \frac{2v_m}{\pi}, \quad v_m = \sqrt{2}V_{s,RMS}$$

$$V_{DC(Load)} = \frac{2v_m}{\pi} = \frac{2(120\sqrt{2})}{\pi} = 108V$$

(b)

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$$

$$I_{DC(Load)} = \frac{108}{10.8} = 10 A$$

(c)

$$I_{DC(diode)} = \frac{I_m}{\pi} \quad , I_m = \frac{v_m}{R}$$

$$I_{DC(Load)} = \frac{15.7}{\pi} = 5A$$

(d)

$$P_{DC(load)} = V_{DC(load)} I_{DC(load)}$$
$$P_{DC(load)} = (108)(10) = 1080Watt$$

(a)

$$\eta = \frac{P_{DC(load)}}{V_{s,RMS} I_{s,RMS}} * 100\% \quad , I_{s,RMS} = \frac{v_m}{\sqrt{2}R} = \frac{120\sqrt{2}}{10.8\sqrt{2}} = 11A$$

$$\eta = \frac{1080}{(120)(11)} * 100\% = 81\%$$

(f)

$$RF = \sqrt{\left(\frac{V_{RMS(Load)}}{V_{DC(Load)}}\right)^2 - 1} = \sqrt{\left(\frac{120}{108}\right)^2 - 1} = 0.484$$

### 2.3.1 Single-phase full-wave bridge uncontrolled rectifier loaded with highly inductive load

Adding an inductance in series with the load resistance changes the current waveform. A basic single-phase full-wave bridge uncontrolled rectifier with resistive and inductance load is shown in Figure 2.9.



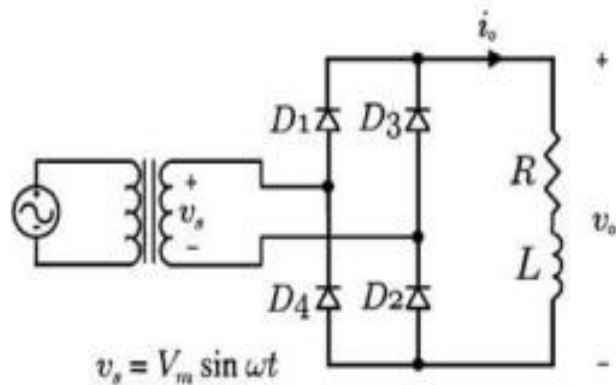


Figure 2.9: A single-phase full-wave bridge uncontrolled rectifier with R-L load.

If L is approximately equal to R, the load current no longer consists of half sine waves, but the average current is still the same as given by equation:

$$I_{DC(Load)} = \frac{2v_m}{\pi R}$$

For the bridge circuit, current is transferred from one pair of diodes to the other pair when the source changes polarity. The voltage across the R-L load is a full-wave rectified sinusoid, as it was for the resistive load.

$$V_{DC(Load)} = \frac{2v_m}{\pi} \quad , \quad V_{RMS(Load)} = \frac{v_m}{\sqrt{2}}$$

In some applications, the load inductance may be relatively large or made large by adding external inductance. If L is much higher than R ( $L \gg R$ ), the load time constant  $L/R$  is very high and can be considered infinity. Consequently, the load current is assumed constant and the circuit behavior is as shown by the waveforms in Figure 2.10.

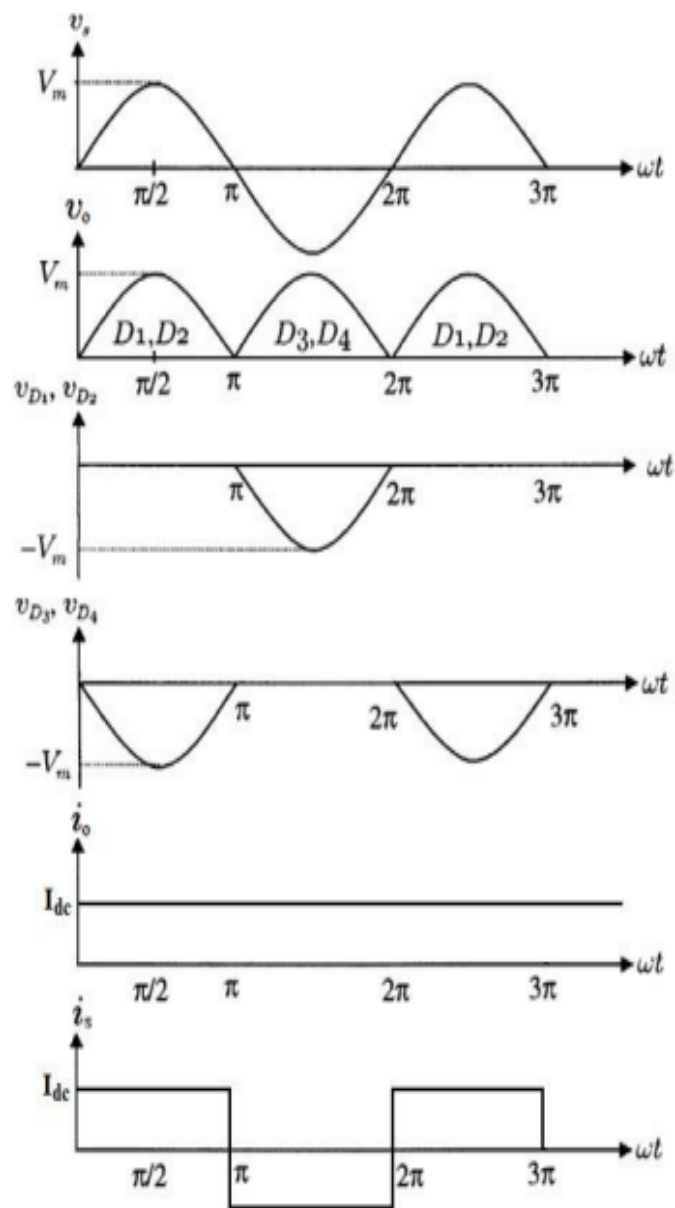


Figure 2.10: The waveforms of the single-phase full-wave bridge uncontrolled rectifier loaded with highly inductive load.

Lecture: 2

Same as the case of resistive load, the average value of the load voltage and current can be calculated as follows:

$$V_{DC(Load)} = \frac{2v_m}{\pi}$$

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$$

$$I_{DC(Load)} = \frac{2v_m}{\pi R}$$

However the rms value of the load voltage can be calculated as follows:

$$V_{RMS(Load)} = \frac{v_m}{\sqrt{2}}$$

Since the load current is essentially constant, its RMS and average values are same:

$$I_{RMS(Load)} = I_{DC(Load)}$$

**Example 4:** The single-phase full-wave bridge uncontrolled rectifier with R-L load is connected to a 120 V source. If the load resistance is 10  $\Omega$  and  $L \gg R$ , find:

- The average load voltage and current.
- The RMS value of load current.
- The average current in each diode.
- The ripple factor.

Solution:

$$V_{s,RMS} = 120 \text{ V}, \quad R = 10 \Omega, \quad L \gg R$$

(a)

$$V_{DC(Load)} = \frac{2v_m}{\pi}, \quad v_m = \sqrt{2}V_{s,RMS}$$

$$V_{DC(Load)} = \frac{2(120\sqrt{2})}{\pi} = 108V$$

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R} = \frac{108}{10} = 10.8A$$

(b)

$$I_{RMS(Load)} = I_{DC(Load)} = 10.8A$$

(c)

$$I_{DC(diode)} = \frac{I_{DC(Load)}}{2} = \frac{10.8}{2} = 5.4A$$


(d)

$$RF = \sqrt{\left(\frac{V_{RMS(Load)}}{V_{DC(Load)}}\right)^2 - 1} = \sqrt{\left(\frac{120}{108}\right)^2 - 1} = 0.484$$

## **Assignment 2**

1. An ideal single-phase source of 240 V, 60 Hz, supplies power to a load resistor of  $R = 100 \Omega$  via a single ideal diode. Determine:
  - (a) The average and RMS values of load current.
  - (b) The power dissipation.
  - (c) The circuit power factor.
  - (d) What must be the rating of the diode?
2. For the circuit shown in Figure below. Neglecting the diode voltage drop, calculate the average load voltage and current, then sketch the output current waveform if (a) the load is a pure resistor of 10 ohms, (b) the load is an inductance of 0.1 H in series with a 10 ohms resistor. Assume the extinction angle  $\beta = 265^\circ$ .

Lecture: 2

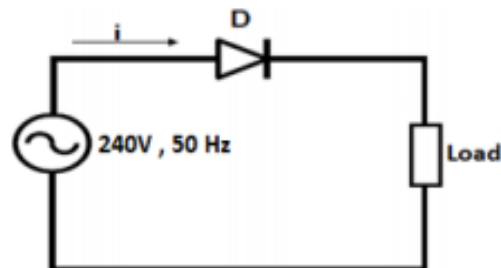

1. A single-phase full-wave uncontrolled bridge rectifier is supplying a highly inductive load ( $L/R$  ratio is very large). If the supply voltage is 220V, 50Hz, and the load resistance  $R=22\ \Omega$ , Calculate:
  - (a) The average output voltage and current.
  - (b) The rms value of the output voltage and current.
  - (c) The rms value of the diode current and the PRV of each diode.
2. In a single-phase full-wave bridge uncontrolled rectifier, the diodes have a reverse recovery time of  $40\ \mu\text{s}$ . If the ac input voltage is 230 V, determine the effect of reverse recovery time on the average output voltage for a supply frequency of (a) 50 Hz and (b) 2.5 kHz.
3. A single-phase full-wave bridge diode rectifier is supplied from 230 V, 50 Hz source. If the load is highly inductive with a resistance of  $R = 10$ . Sketch  $v_{in}$ ,  $v_o$ ,  $v_{D2}$ ,  $v_{D3}$ ,  $i_o$  and  $i_s$  waveforms, and then determine:
  - (a) The average values of output voltage and output current.
  - (b) The average and RMS values of diode current.
  - (c) The ripple factor.

## 2.4 Three-Phase Half-Wave Uncontrolled Rectifier

A basic three-phase half-wave uncontrolled rectifier circuit with resistive load is shown in Figure 2.11. The rectifier is fed from an ideal 3-phase supply through delta-star transformer.

The diode in a particular phase conducts during the period when the voltage on that phase is higher than that on the other two phases. For example: from  $\pi/6$  to  $5\pi/6$ ,  $D_1$  has a more positive voltage at its anode, in this period  $D_2$  and  $D_3$  are off. The neutral wire provides a return path to the load current.

Unlike the single-phase rectifier circuit, the conduction angle of each diode is  $2\pi/3$ , instead of  $\pi$ . The voltage and current waveforms on resistive load and the voltage and current waveforms on  $D_1$  are shown in Figure 2.12.

### Assignment 3

1. A heavily inductive load of  $R = 5 \Omega$  is to be supplied with a DC voltage of 200 V, using three-phase bridge rectifier. Calculate:
  - (a) The DC load current.
  - (b) The RMS current of any diode.
  - (c) The transformer secondary phase current.
  - (d) The transformer secondary line voltage.
  - (e) PRV of any diode.
  
2. Repeat Q1 above if the rectifier is three-phase half-wave type.

#### 2.6 Single-Phase Half-Wave Controlled Rectifier

A way to control the output of a single-phase half-wave rectifier is to use a thyristor instead of a diode. A basic single-phase half-wave controlled rectifier with a resistive load is shown in Figure 2.16.

During the positive half cycle of the input voltage, thyristor T1 is forward biased and current flows through the load when the thyristor is fired (at  $wt = \alpha$ ). The thyristor conducts only when the anode is positive with respect to cathode (forward biased), and a positive pulse signal is applied to the gate, otherwise, it remains in the forward blocking state and blocks the flow of the load current.

In the negative half cycle (i.e., at  $wt = \pi - 2\pi$ ), the thyristor is in the reverse biased condition and no current flows through the load. Thus, varying the firing angle at which the thyristor starts conducting in positive half cycle controls the



average DC output voltage. The voltage and current waveforms on resistive load and the voltage waveform on the thyristor are shown in Figure 2.17.

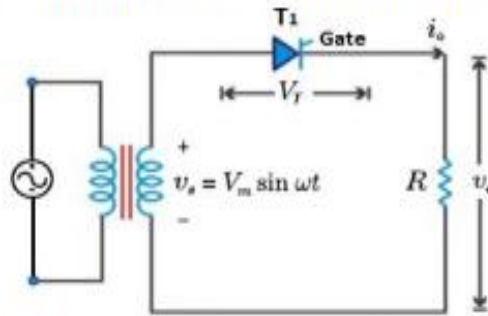


Figure 2.16: A basic single-phase half-wave controlled rectifier with a resistive load.

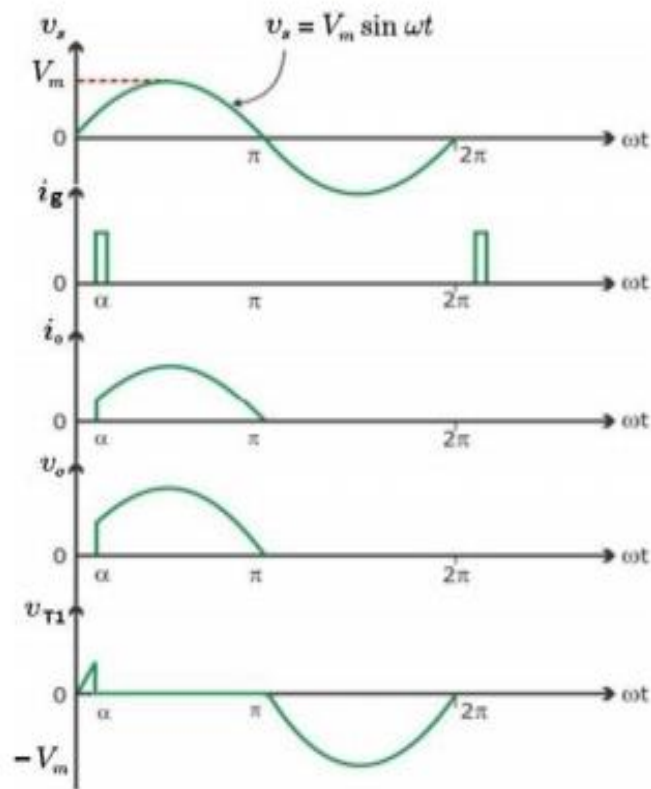


Figure 2.17: The waveforms of the single-phase half-wave controlled rectifier with a resistive load.



$$V_{DC(Load)} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{2\pi} (1 + \cos(\alpha))$$

$$V_{DC(Load)} = \frac{V_m}{2\pi} (1 + \cos(\alpha))$$

The average value of output current,  $I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$

$$V_{RMS(Load)} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d\omega t} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$I_{RMS(Load)} = \frac{V_{RMS(Load)}}{R}$$

**Example 7:** The single-phase half wave rectifier has a purely resistive load of 10  $\Omega$  and the delay angle is  $\alpha = \pi/2$ . If the supply voltage is 220 V, determine the DC load voltage and current.

**Solution:**

$$V_{DC(Load)} = \frac{V_m}{2\pi} (1 + \cos(\alpha)) = \frac{220\sqrt{2}}{2\pi} (1 + \cos(90)) = 49.5V$$

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R} = \frac{49.5}{10} = 4.95A$$

## 2.7 Single-Phase Full-Wave Bridge Controlled Rectifier

A basic single-phase full-wave bridge controlled rectifier with a resistive load is shown in Figure 2.18. This type of rectifier uses four thyristors to control the average load voltage.

Thyristors T1 and T2 must be fired at the same time during the positive half cycle of the source voltage to allow conduction of current. Alternatively, thyristors T3 and T4 must be fired at the same time during the negative half cycle of the source voltage.

The voltage and current waveforms on resistive load, and the voltage waveform on the thyristor T1 and T2 are shown in Figure 2.19.

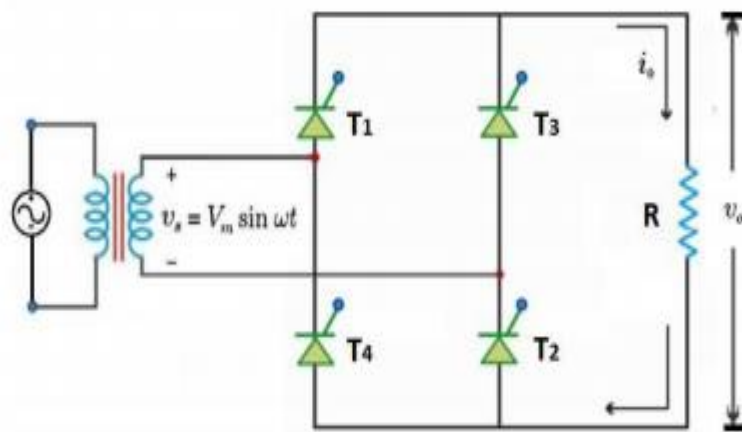


Figure 2.18: A single-phase full-wave bridge controlled rectifier with a resistive load.

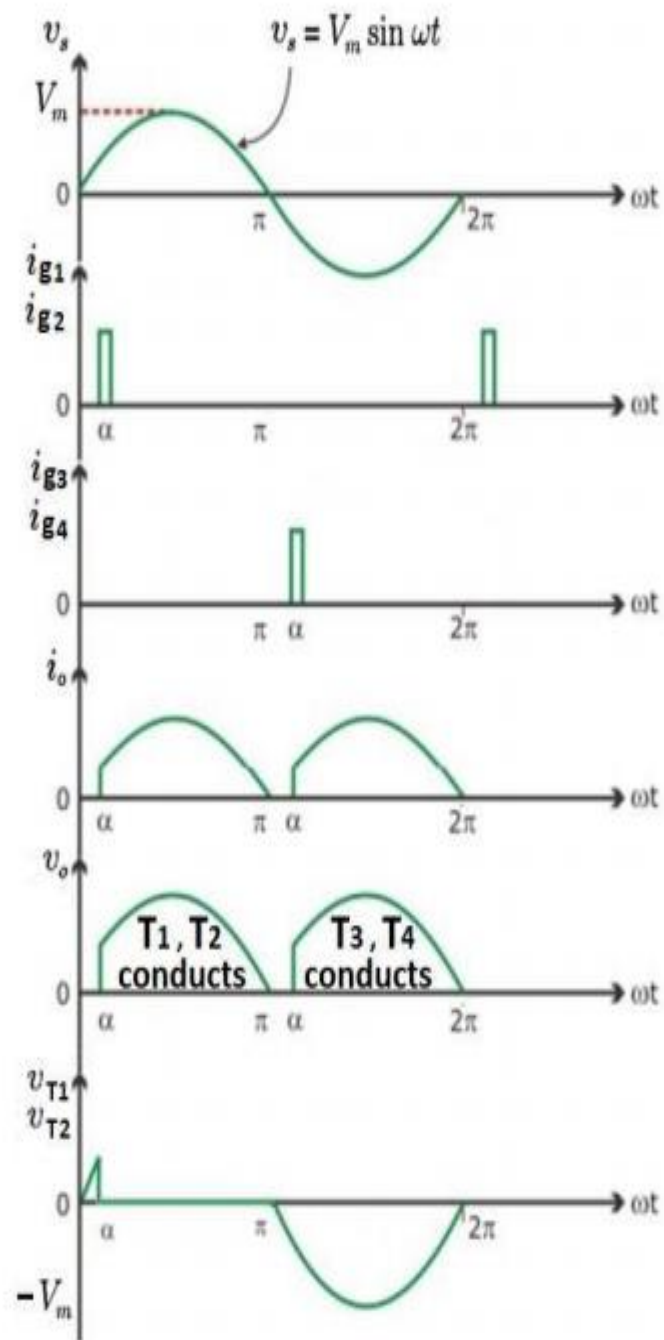


Figure 2.19: The waveforms of the single-phase full-wave bridge uncontrolled rectifier with a resistive load.

$$V_{DC(Load)} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{\pi} (1 + \cos(\alpha))$$

$$V_{DC(Load)} = \frac{V_m}{\pi} (1 + \cos(\alpha))$$

The average value of output current,  $I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$

$$V_{RMS(Load)} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d\omega t} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

$$I_{RMS(Load)} = \frac{V_{RMS(Load)}}{R}$$

**Example 8:** The single-phase full-wave controlled bridge rectifier has an ac input of 120 V at 60 Hz and a 5  $\Omega$  load resistor. The delay angle is 40°. Determine the average current in the load.

**Solution:**

$$V_{DC(Load)} = \frac{V_m}{\pi} (1 + \cos(\alpha))$$

$$V_{DC(Load)} = \frac{120\sqrt{2}}{\pi} (1 + \cos(40^\circ)) = 95.4V$$

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R} = \frac{95.4V}{5\Omega} = 19.1A$$

The behavior of the full-wave controlled rectifier with R-L load (highly inductive

load) is shown in Figure 2.20. The high inductance generates a perfectly filtered current and the rectifier behaves like a current source. With continuous load current, thyristors T1 and T2 remain in the ON-state beyond the positive half-wave of the source voltage. For this reason, the load voltage can have a negative instantaneous value.

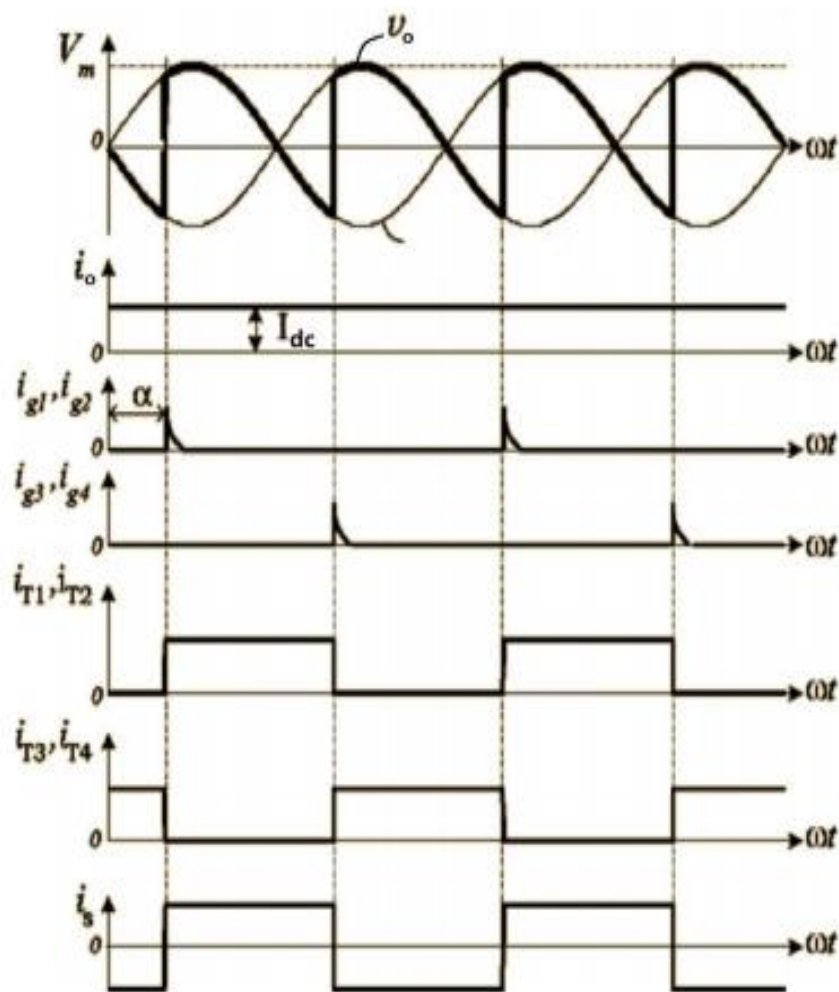


Figure 2.20: The waveforms of the single-phase full-wave bridge controlled rectifier loaded with highly inductive load.

$$V_{DC(Load)} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin(\omega t) d\omega t = \frac{2V_m}{\pi} \cos(\alpha)$$

$$V_{DC(Load)} = \frac{2V_m}{\pi} \cos(\alpha)$$


The average value of output current,  $I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$

$$V_{RMS(Load)} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d\omega t} = \frac{V_m}{\sqrt{2}}$$

$$I_{RMS(Load)} = I_{DC(Load)}$$

#### Assignment 4

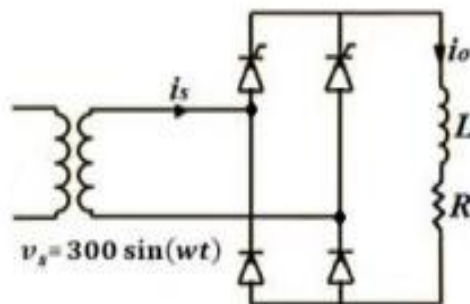1. For the rectifier circuit shown in Figure below,  $\alpha = 90^\circ$ , L is very high.
  - (a) Trace  $i_s$  waveform.
  - (b) Calculate  $V_{load (mean)}$ .
  - (c) If  $L = 0$ , repeat (a) and (b) above.



2. A resistive load of  $R = 100$  is to be supplied with a DC voltage of 40V using single-phase half-wave rectifier. If the supply voltage is 120 V,


- (a) Calculate the required delay angle.
- (b) Trace the thyristor current and voltage waveforms.

3. For the circuit shown in Figure below, TH is triggered reference to each zero cross over point, If  $\alpha = 60^\circ$ ,

(a) Trace  $i_s$  and  $i_{TH}$  waveforms.

(b) Calculate  $V_{\text{load(average)}}$ .

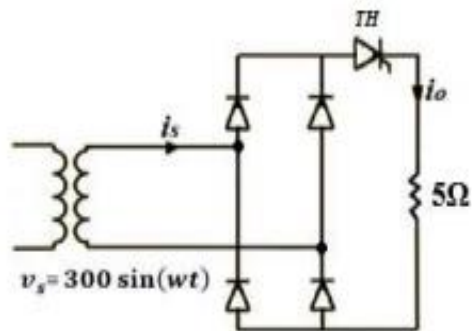(c) How much  $\alpha$  must be varied to compensate for 5% increase of the supply voltage.





Lecture: 1

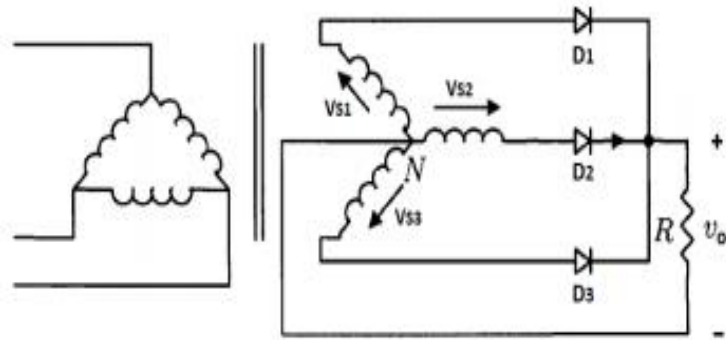


Figure 2.11: A three-phase half-wave uncontrolled rectifier with resistive load.

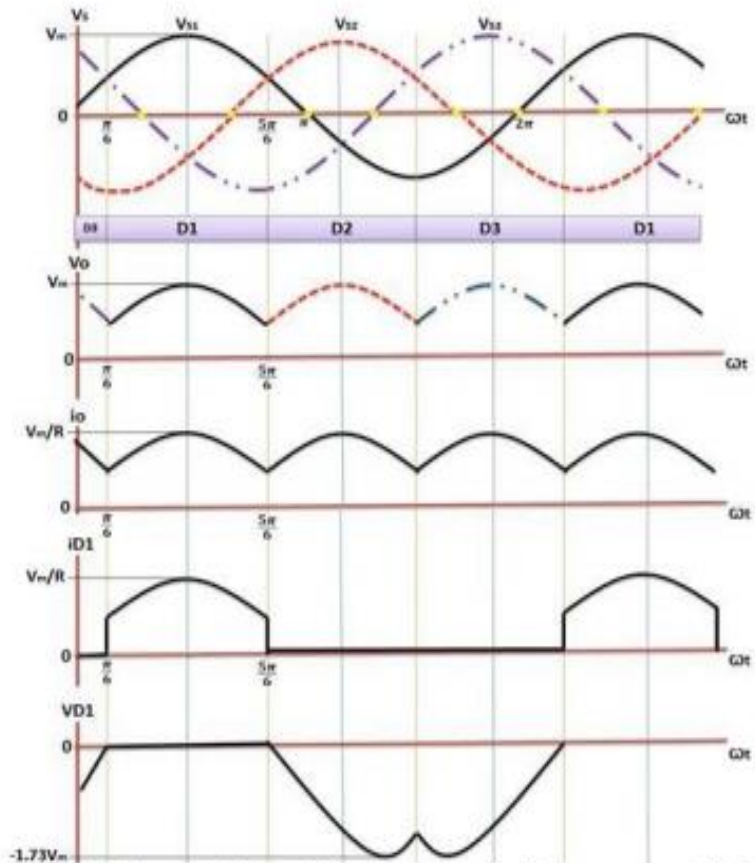


Figure 2.12: The waveforms of the three-phase half-wave uncontrolled rectifier with a resistive load.



$$V_{line} = \sqrt{3}V_{phase}$$

The average value of the load voltage:

$$V_{DC(Load)} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} v_m \sin \omega t d\omega t$$

$$V_{DC(Load)} = \frac{3\sqrt{3}v_{m(phase)}}{2\pi}$$

The average value of the load current:

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$$

$$I_{DC(Load)} = \frac{3\sqrt{3}v_{m(phase)}}{2\pi R}$$

The rms value of the output voltage and current:

$$V_{RMS(Load)} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} [v_m \sin \omega t]^2 d\omega t} = 0.84 v_{m(phase)}$$

$$I_{RMS(Load)} = \frac{V_{RMS(Load)}}{R}$$

Adding an inductance in series with the load resistance changes the current waveform. If L is much higher than R (L >>> R), the load time constant L/R is very high and can be considered infinity. Consequently, the load current is assumed constant as shown by the waveforms in Figure 2.13.

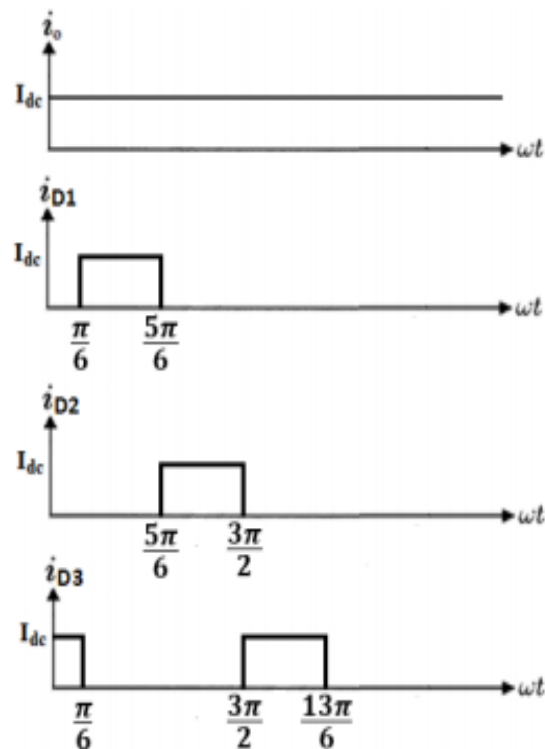


Figure 2.13: The current waveforms of the three-phase half-wave uncontrolled rectifier loaded with highly inductive load.

**Example 5:** Power is supplied to heavily inductive load from a three-phase supply, using a three-phase half-wave rectifier. If the supply phase voltage is 220 V and the resistance of the load is  $100 \Omega$ , determine the DC load voltage and current. Then,

- (a) Sketch the output load voltage waveform.
- (b) Sketch D1 current waveform.

**3 Solution:**


$$V_{i, \text{RMS phase}} = 220 \text{ V}, \quad R = 100 \Omega, \quad L \gg R$$

$$V_{DC(Load)} = \frac{3\sqrt{3}v_{m(phase)}}{2\pi}, \quad v_{m(phase)} = 220\sqrt{2}$$

$$V_{DC(Load)} = \frac{(3\sqrt{3})(220\sqrt{2})}{2\pi} = 257.4V$$

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$$
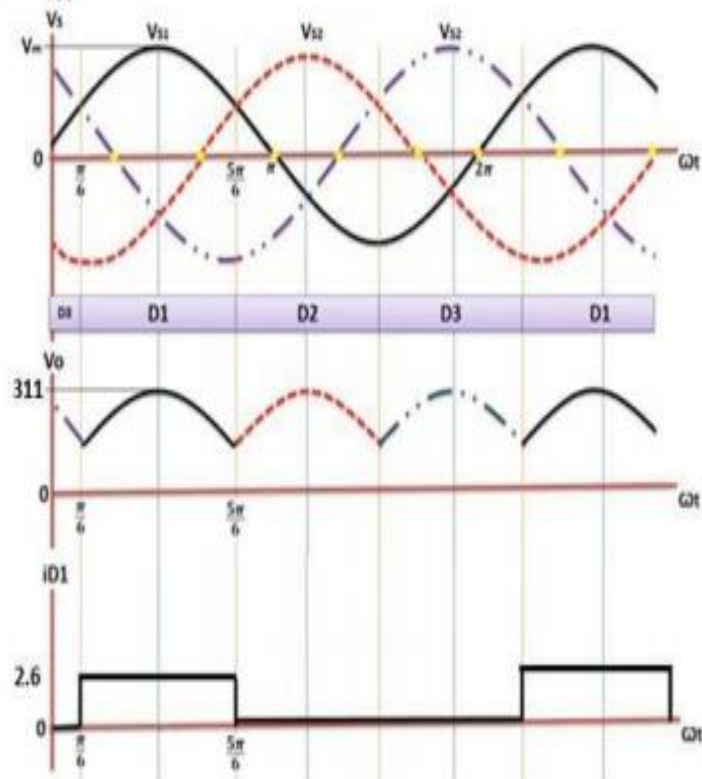
$$I_{DC(Load)} = \frac{257.4V}{100} = 2.6A$$



### 3.4 Three-Phase Full-Wave (Bridge) Uncontrolled Rectifier

A basic three-phase Full-wave uncontrolled rectifier circuit is shown in Figure 2.14. The rectifier is fed from an ideal 3-phase supply through delta-star transformer. The principle of operation of this rectifier can be explained as follows:

- Each three-phase line connects between pair of diodes. One to route power to positive (+) side of load, and other to route power to negative (-) side of load.
- Only one diode in the top half of the bridge may conduct at one time (D1, D3, or D5). The diode that is conducting will have its anode connected to the phase voltage that is highest at that instant.
- Only one diode in the bottom half of the bridge may conduct at one time (D2, D4, or D6). The diode that is conducting will have its cathode connected to the phase voltage that is lowest at that instant.
- There are six combinations of line-to-line voltages (three phases taken two at a time). Considering one period of the source to be  $2\pi$ , a transition of the highest line-to-line voltage must take place every  $2\pi/6 = \pi/3$ . Because of the six transitions that occur for each period of the source voltage, the circuit is called a six-pulse rectifier.

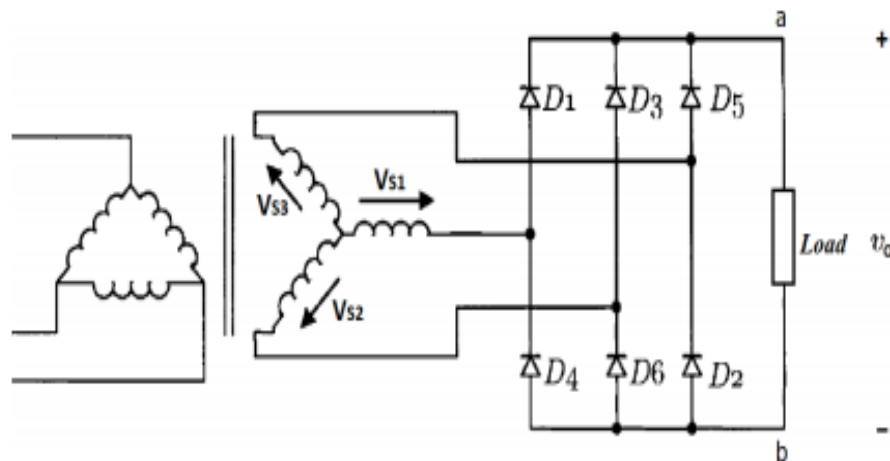


Figure 2.14: A three-phase full-wave uncontrolled rectifier.

Similar to the three-phase rectifier circuit, the conduction angle of each diode is  $2\pi/3$ . If  $L$  is much higher than  $R$  ( $L \gg R$ ), the load time constant  $L/R$  is very high

and can be considered infinity. Consequently, the load current is assumed constant. The current and voltage waveforms of the three-phase full-wave uncontrolled rectifier loaded with highly inductive load are shown in Figure 2.15.

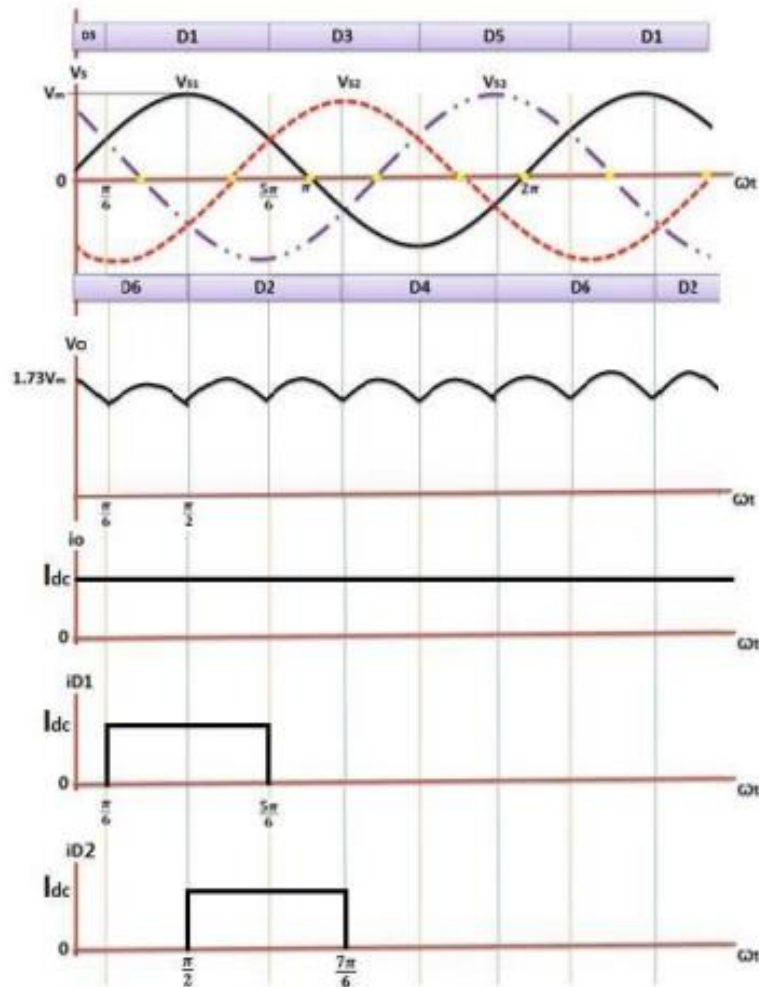


Figure 2.15: The current and voltage waveforms of the three-phase full-wave uncontrolled rectifier loaded with highly inductive load.

The average value of the load voltage:

$$V_{DC(Load)} = \frac{3}{\pi} \int_{\pi/6}^{\pi/2} \sqrt{3}v_m \sin\left(\omega t + \frac{\pi}{6}\right) d\omega t = \frac{3}{\pi} \int_{\pi/3}^{2\pi/3} \sqrt{3}v_m \sin \omega t d\omega t$$

$$V_{DC(Load)} = \frac{3\sqrt{3}v_{m(phase)}}{\pi}$$

The average value of the load current:

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$$

$$I_{DC(Load)} = \frac{3\sqrt{3}v_{m(phase)}}{\pi R}$$

The rms value of the output voltage and current:

$$V_{RMS(Load)} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} \left[\sqrt{3}v_m \sin\left(\omega t + \frac{\pi}{6}\right)\right]^2 d\omega t} = 1.655v_{m(phase)}$$

$$I_{RMS(Load)} = I_{DC(Load)}$$

**Example 6:** Power is supplied to heavily inductive load from a three-phase supply, using a three-phase bridge rectifier. If the supply phase voltage is 220 V and the resistance of the load is 10  $\Omega$ , determine the DC load voltage and current. Then, sketch the output load voltage, the load current, and D4 current waveforms.


$$V_{i,RMS(phase)} = 220 \text{ V}, R = 10 \Omega, L \gg R$$

$$V_{DC(Load)} = \frac{3\sqrt{3}v_{m(phase)}}{\pi}, \quad v_{m(phase)} = 220\sqrt{2}$$

$$V_{DC(Load)} = \frac{(3\sqrt{3})(220\sqrt{2})}{\pi} = 514.9 \text{ V}$$

$$I_{DC(Load)} = \frac{V_{DC(Load)}}{R}$$
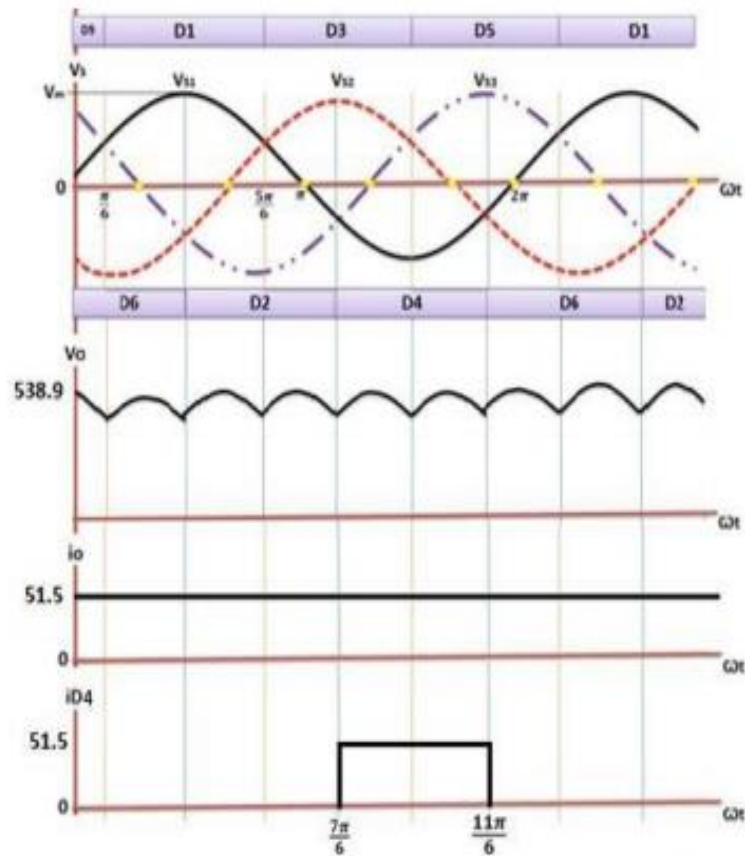
$$I_{DC(Load)} = \frac{514.9V}{10} = 51.49A$$



### Assignment 3

1. A heavily inductive load of  $R = 5 \Omega$  is to be supplied with a DC voltage of 200 V, using three-phase bridge rectifier. Calculate:

(a) The DC load current.



- (b) The RMS current of any diode.
  - (c) The transformer secondary phase current.
  - (d) The transformer secondary line voltage.
  - (e) PRV of any diode.
2. Repeat Q1 above if the rectifier is three-phase half-wave type.

### 3.5 Single-Phase Half-Wave Controlled Rectifier

- 4 A way to control the output of a single-phase half-wave rectifier is to use a thyristor instead of a diode. A basic single-phase half-wave controlled rectifier with a resistive load is shown in Figure 2.16.
- 5 During the positive half cycle of the input voltage, thyristor T1 is forward biased and current flows through the load when the thyristor is fired (at  $wt = \alpha$ ). The thyristor conducts only when the anode is positive with respect to cathode (forward biased), and a positive pulse signal is applied to the gate, otherwise, it remains in the forward blocking state and blocks the flow of the load current.
- 6 In the negative half cycle (i.e., at  $wt = \pi - 2\pi$ ), the thyristor is in the reverse biased condition and no current flows through the load. Thus, varying the firing angle at which the thyristor starts conducting in positive half cycle controls the average DC output voltage. The voltage and current waveforms on resistive load and the voltage waveform on the thyristor are shown in Figure 2.17.