

## Modeling of shunt DC motor

As mentioned previously, self-excited DC machines are classified to shunt-connected, series-connected and compound DC machines. In this lecture, the model of DC motor with field winding connected in parallel to the armature winding is presented.

### Electrical and mechanical equations of shunt-connected DC machines

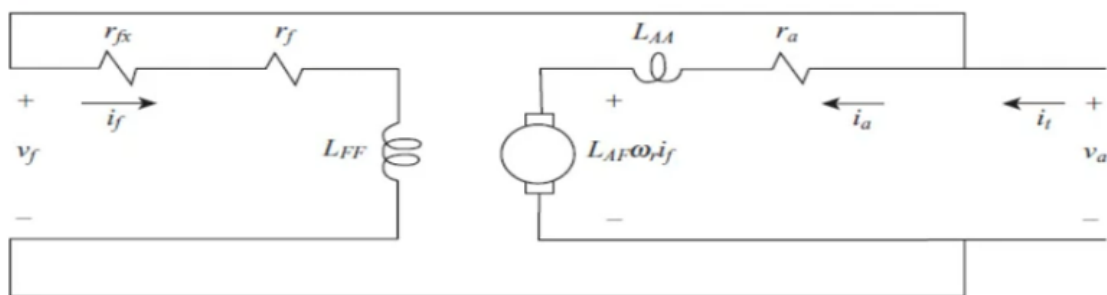


Fig. (1) Equivalent circuit of Shunt-connected DC machine [2]

1. Find the equations which describe the system.

$$v_f = v_a \quad (1)$$

$$v_a = \left( r_a + \frac{dL_{AA}}{dt} \right) i_a + \omega_r L_{AF} i_f \quad (2)$$

$$v_f = \left( r_f + \frac{dL_{FF}}{dt} \right) i_f \quad (3)$$

$$T_e = J \frac{d\omega_r}{dt} + B_m \omega_r + T_l \quad (4.a)$$

$$T_e = L_{AF} i_a i_f \quad (4.b)$$

$$V_a(s) = r_a I_a(s) + sL_{AA}I_a + \omega_r L_{AF}I_f$$

$$\therefore I_a(s) = \frac{1}{(r_a + sL_{AA})} (V_a(s) - \omega_r L_{AF}I_f) \quad (5.a)$$

$$V_f(s) = (r_f + sL_{FF})I_f(s)$$

$$\therefore I_f(s) = \frac{1}{(r_f + sL_{FF})} V_f(s) \quad (5.b)$$

$$T_e(s) = (sJ + B_m)\omega_r(s) + T_l(s) \quad , \quad T_e(s) = L_{AF}I_f I_a(s)$$

$$\therefore \omega_r(s) = \frac{1}{(sJ + B_m)} (L_{AF}I_f I_a(s) - T_l(s)) \quad (5.c)$$

```

1 - clear;
2 - clc
3 - Bm=0.0000010;
4 - Ti=2.5;
5 - Va=24;
6 - Vf=12;
7 - Ra=0.013;
8 - Rf=1.5;
9 - LAA=0.01;
10 - LFF=0.16;
11 - LAF=0.004;
12 - J=0.21;
13

```

