

Ac Bridge and their Application:

The ac bridge is a natural outgrowth of the dc bridge and in its basic form consists of four bridge arms, a source of excitation, and a null ac detector. For measurements at low frequencies, the power line may serve as the source of excitation; but at higher frequencies an oscillator generally supplies the excitation voltage. The null ac detector in its cheapest effective form consists of a pair of headphones or may be oscilloscope.

The balance condition is reached when the detector response is zero or indicates null. Then $V_{AC} = 0$ and $V_{Z1} = V_{Z2}$

$$V_{Z1} = V_{in} \frac{Z_1}{Z_1 + Z_3}$$

$$V_{Z2} = V_{in} \frac{Z_2}{Z_2 + Z_4} \quad \text{thus}$$

$$\boxed{Z_1 Z_4 = Z_2 Z_3} \quad \text{is the balance equation}$$


$$\text{Or } \boxed{Y_1 Y_4 = Y_2 Y_3}$$

The balance equation can be written in complex form as:

$$(Z_1 \angle \theta_1)(Z_4 \angle \theta_4) = (Z_2 \angle \theta_2)(Z_3 \angle \theta_3)$$

$$\text{And } (Z_1 Z_4 \angle \theta_1 + \theta_4) = (Z_2 Z_3 \angle \theta_2 + \theta_3)$$

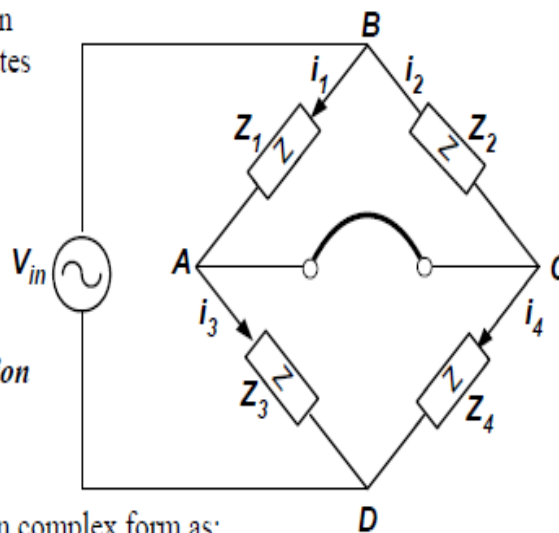So two conditions must be met simultaneously when balancing an ac bridge



Magnitude balance: $Z_1 Z_4 = Z_2 Z_3$

Phase balance: $\angle \theta_1 + \angle \theta_4 = \angle \theta_2 + \angle \theta_3$

Review on Ac Impedance:

a) In series connection


Impedance = resistance $\pm j$ reactance

$$Z_L = R + jXL \quad \text{and} \quad Z_L = R + j\omega L$$

$$Z_C = R - jXC \quad \text{and} \quad Z_C = R - j\frac{1}{\omega C}$$

Conversion from polar to rectangular
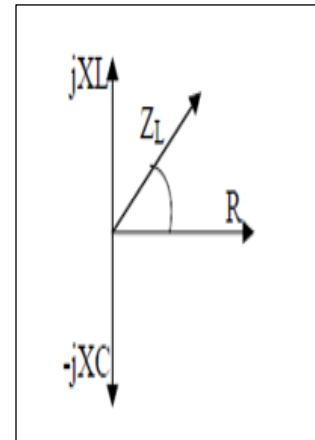
$$Z \angle \theta \quad \text{in polar form} \quad R = Z \cos \theta$$



$$X = Z \sin \theta \quad \text{become} \quad Z = R \pm jX$$

Conversion from rectangular to polar

$$Z = R \pm jX \quad \text{in rectangular form} \quad Z = \sqrt{R^2 + X^2} \quad \theta = \tan^{-1} \frac{X}{R} \quad \tan \theta = \frac{X}{R}$$


b) In parallel connection

Admittance = conductance $\pm j$ susceptance

$$Y_L = G - jB_L \quad \text{and} \quad Y_L = \frac{1}{R} - j\frac{1}{\omega L}$$

$$Y_C = G + jB_C \quad \text{and} \quad Y_C = \frac{1}{R} + j\omega C$$
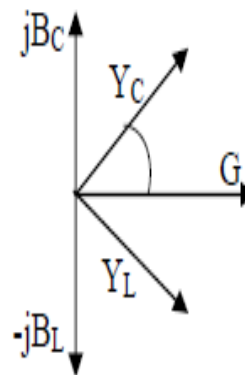
$$\tan \theta = \frac{B_C}{G} = \frac{\frac{1}{X_C}}{\frac{1}{R}} = \frac{\omega C}{\frac{1}{R}} = \omega RC$$



Example The impedance of the basic ac bridge are given as follows:

$$\begin{array}{ll} Z_1 = 100 \Omega \angle 80^\circ \text{ (inductive impedance)} & Z_3 = 400 \angle 30^\circ \Omega \text{ (inductive impedance)} \\ Z_2 = 250 \Omega \text{ (pure resistance)} & Z_4 = \text{unknown} \end{array}$$

Determine the constants of the unknown arm.

SOLUTION The first condition for bridge balance requires that

$$Z_4 = \frac{Z_2 Z_3}{Z_1} = \frac{250 \times 400}{100} = 1,000 \Omega$$

The second condition for bridge balance requires that the sum of the phase angles of opposite arms be equal, therefore


$$\angle \theta_4 = \angle \theta_2 + \angle \theta_3 - \angle \theta_1 = 0 + 30 - 80 = -50^\circ$$

Hence the unknown impedance Z_4 can be written in polar form as

$$Z_4 = 1,000 \Omega \angle -50^\circ$$

Indicating that we are dealing with a capacitive element, possibly consisting of a series combination of a resistor and a capacitor.

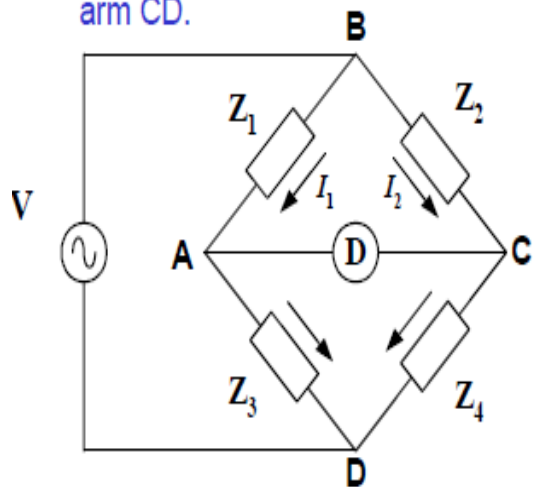Example an ac bridge is in balance with the following constants: arm AB, $R = 200 \Omega$ in series with $L = 15.9 \text{ mH}$; arm BC, $R = 300 \Omega$ in series with $C = 0.265 \mu\text{F}$; arm CD, unknown; arm DA, $= 450 \Omega$. The oscillator frequency is 1 kHz. Find the constants of arm CD.



SOLUTION

$$Z_1 = R + j\omega L = 200 + j100 \Omega$$

$$Z_2 = R + 1/j\omega C = 300 - j600 \Omega$$

$$Z_3 = R = 450 \Omega$$

$$Z_4 = \text{unknown}$$

The general equation for bridge balance states that $Z_1 Z_4 = Z_2 Z_3$

$$Z_4 = \frac{Z_2 Z_3}{Z_1} = \frac{450 \times (200 + j100)}{(300 - j600)} = j150 \Omega$$

This result indicates that Z_4 is a pure inductance with an inductive reactance of 150Ω at a frequency of 1 kHz. Since the inductive reactance $X_L = 2\pi fL$, we solve for L and obtain $L = 23.9 \text{ mH}$

Example

For the following bridge find Z_x ?

The balance equation $Z_1 Z_4 = Z_2 Z_3$

$$Z_1 = R = 450\Omega$$

$$Z_2 = R + \frac{1}{j\omega C} = R - \frac{j}{\omega C}$$

$$Z_2 = 300 - j600$$


$$Z_3 = R + j\omega L$$

$$Z_3 = 200 + j100$$

$$Z_4 = Z_x = \text{unknown}$$

$$Z_4 = \frac{Z_2 Z_3}{Z_1} \quad Z_4 = \frac{(300 - j600)(200 + j100)}{450} = 266.6 - j200$$
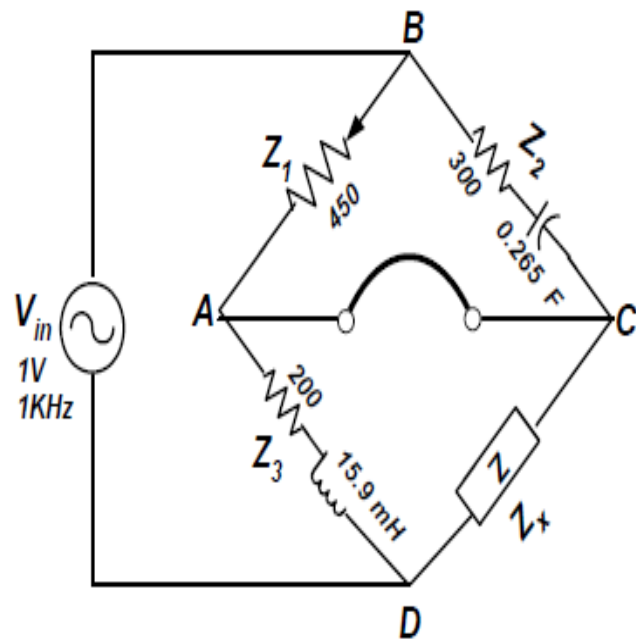
$$R = 266.6\Omega \quad C = \frac{1}{2\pi F \times 200} = 0.79\mu F$$



Comparison Bridge: Capacitance

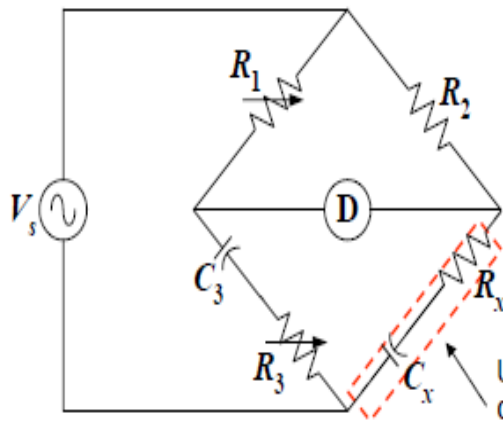


Diagram of Capacitance Comparison Bridge

- Measure an unknown inductance or capacitance by comparing with it with a known inductance or capacitance.

At balance point: $Z_1 Z_x = Z_2 Z_3$

where $Z_1 = R_1$; $Z_2 = R_2$; and $Z_3 = R_3 + \frac{1}{j\omega C_3}$

$$R_1 \left(R_x + \frac{1}{j\omega C_x} \right) = R_2 \left(R_3 + \frac{1}{j\omega C_3} \right)$$

Separation of the real and imaginary terms yields:

$$R_x = \frac{R_2 R_3}{R_1}$$

and

$$C_x = C_3 \frac{R_1}{R_2}$$

- Frequency independent
- To satisfy both balance conditions, the bridge must contain two variable elements in its configuration.

Comparison Bridge: Inductance

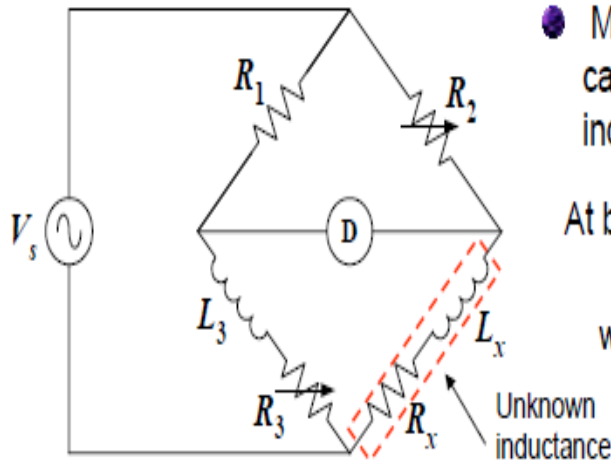


Diagram of Inductance Comparison Bridge

- Measure an unknown inductance or capacitance by comparing with it with a known inductance or capacitance.

At balance point: $Z_1 Z_x = Z_2 Z_3$

where $Z_1 = R_1$; $Z_2 = R_2$; and $Z_3 = R_3 + j\omega L_3$

$$R_1 (R_x + j\omega L_x) = R_2 (R_3 + j\omega L_3)$$

Separation of the real and imaginary terms yields:

$$R_x = \frac{R_2 R_3}{R_1}$$

and

$$L_x = L_3 \frac{R_2}{R_1}$$

- Frequency independent
- To satisfy both balance conditions, the bridge must contain two variable elements in its configuration.