

Comparison Bridge: Capacitance

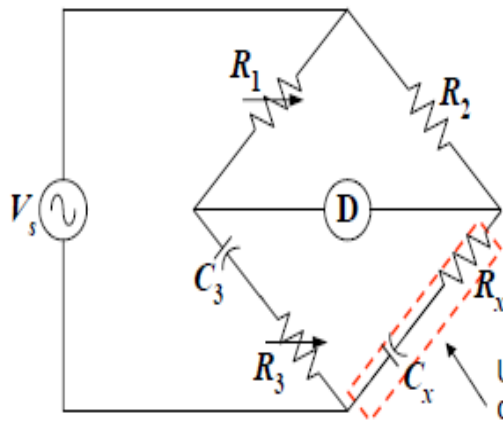


Diagram of Capacitance Comparison Bridge

- Measure an unknown inductance or capacitance by comparing with it with a known inductance or capacitance.

At balance point: $Z_1 Z_x = Z_2 Z_3$

where $Z_1 = R_1$; $Z_2 = R_2$; and $Z_3 = R_3 + \frac{1}{j\omega C_3}$

$$R_1 \left(R_x + \frac{1}{j\omega C_x} \right) = R_2 \left(R_3 + \frac{1}{j\omega C_3} \right)$$

Separation of the real and imaginary terms yields:

$$R_x = \frac{R_2 R_3}{R_1}$$

and

$$C_x = C_3 \frac{R_1}{R_2}$$

- Frequency independent
- To satisfy both balance conditions, the bridge must contain two variable elements in its configuration.

Comparison Bridge: Inductance

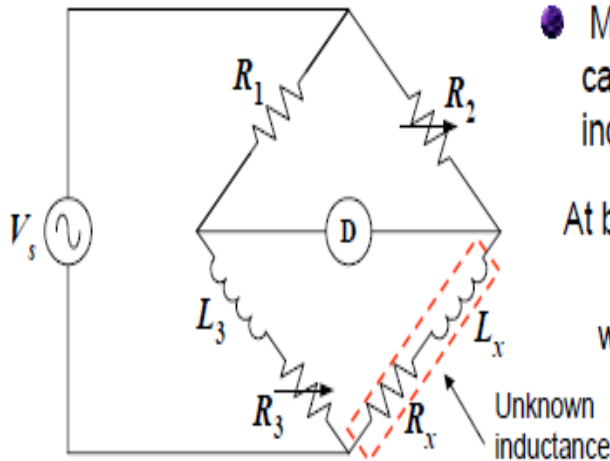


Diagram of Inductance Comparison Bridge

- Measure an unknown inductance or capacitance by comparing with it with a known inductance or capacitance.

At balance point: $Z_1 Z_x = Z_2 Z_3$

where $Z_1 = R_1$; $Z_2 = R_2$; and $Z_3 = R_3 + j\omega L_3$

$$R_1 (R_x + j\omega L_x) = R_2 (R_3 + j\omega L_3)$$

Separation of the real and imaginary terms yields:


$$R_x = \frac{R_2 R_3}{R_1}$$

and

$$L_x = L_3 \frac{R_2}{R_1}$$

- Frequency independent
- To satisfy both balance conditions, the bridge must contain two variable elements in its configuration.

Maxwell Bridge

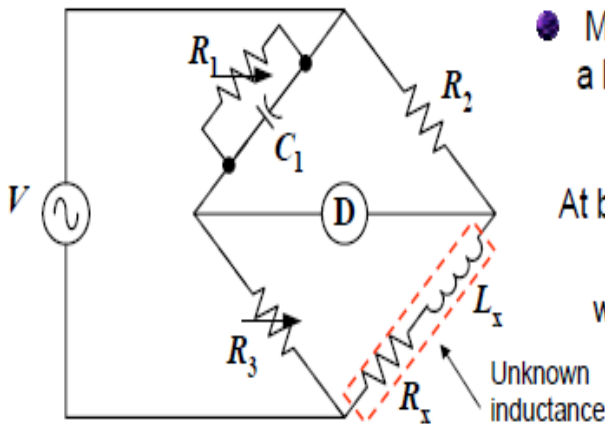

- Measure an unknown inductance in terms of a known capacitance

At balance point: $Z_x = Z_2 Z_3 Y_1$

where $Z_2 = R_2$; $Z_3 = R_3$; and $Y_1 = \frac{1}{R_1} + j\omega C_1$

$$Z_x = R_x + j\omega L_x = R_2 R_3 \left(\frac{1}{R_1} + j\omega C_1 \right)$$

Diagram of Maxwell Bridge

Separation of the real and imaginary terms yields:

$$R_x = \frac{R_2 R_3}{R_1}$$

and $L_x = R_2 R_3 C_1$

- Frequency independent
- Suitable for Medium Q coil (1-10), impractical for high Q coil: since R_1 will be very large.

EXAMPLE

A Maxwell-Wien bridge as shown in below operates at a supply frequency of 100Hz used to measure inductive impedance. The bridge

balanced at the following values:

$$C_1 = 0.01\mu\text{F}, R_1 = 470\Omega, R_2 = 2.2\text{k}\Omega \text{ and } R_3 = 100\Omega$$

Find the series resistance and inductance and determine its Q -factor.

SOLUTION

$$R_s = \frac{R_2 R_3}{R_1} = \frac{2.2\text{k} \times 100}{470} = 468.1\Omega$$

$$L_s = C_1 R_2 R_3 = 0.01\mu \times 2.2\text{k} \times 100 = 2.2\text{mH}$$

