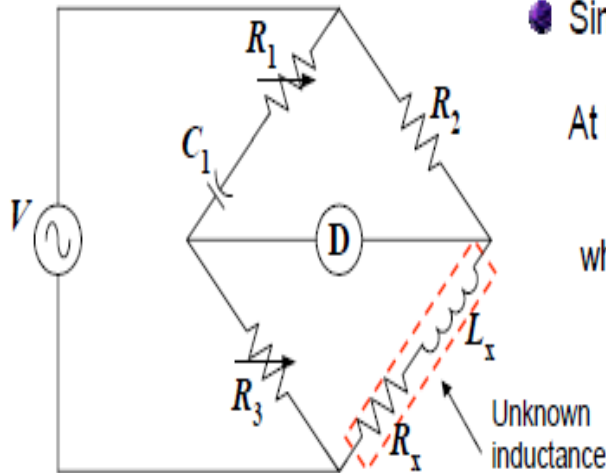


Hay Bridge



• Similar to Maxwell bridge: but R_1 series with C_1

At balance point: $Z_1 Z_x = Z_2 Z_3$

where $Z_1 = R_1 - \frac{j}{\omega C_1}$; $Z_2 = R_2$; and $Z_3 = R_3$

$$\left(R_1 + \frac{1}{j\omega C_1} \right) (R_x + j\omega L_x) = R_2 R_3$$

Diagram of Hay Bridge

which expands to $R_1 R_x + \frac{L_x}{C_1} - \frac{jR_x}{\omega C_1} + j\omega L_x R_1 = R_2 R_3$


$$\begin{cases} R_1 R_x + \frac{L_x}{C_1} = R_2 R_3 \dots\dots\dots (1) \\ \frac{R_x}{\omega C_1} = \omega L_x R_1 \dots\dots\dots (2) \end{cases}$$

Solve the above equations simultaneously

$$R_x = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{1 + \omega^2 C_1^2 R_1^2}$$

and
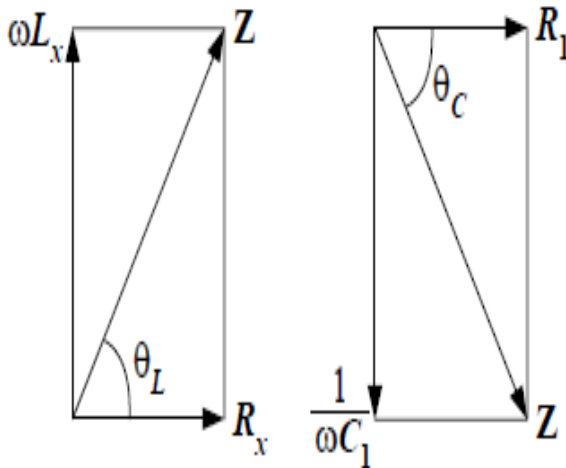
$$L_x = \frac{R_2 R_3 C_1}{1 + \omega^2 C_1^2 R_1^2}$$



$$\tan \theta_L = \frac{X_L}{R} = \frac{\omega L_x}{R_x} = Q$$

$$\tan \theta_C = \frac{X_C}{R} = \frac{1}{\omega C_1 R_1}$$

$$\tan \theta_L = \tan \theta_C \text{ or } Q = \frac{1}{\omega C_1 R_1}$$

Phasor diagram of arm 4 and 1

Thus, L_x can be rewritten as

$$L_x = \frac{R_2 R_3 C_1}{1 + (1/Q^2)}$$

For high Q coil (> 10), the term $(1/Q)^2$ can be neglected

$$L_x \approx R_2 R_3 C_1$$


lecture 14

EXAMPLE

Calculate the inductance and resistance of the network that causes a **Hay bridge** as shown in figure below to null with the following component values: $\omega=3000\text{rad/s}$, $C_1=0.1\text{nF}$, $R_1=20\text{k}\Omega$, $R_2=10\text{k}\Omega$ and $R_3=1\text{k}\Omega$.

SOLUTION

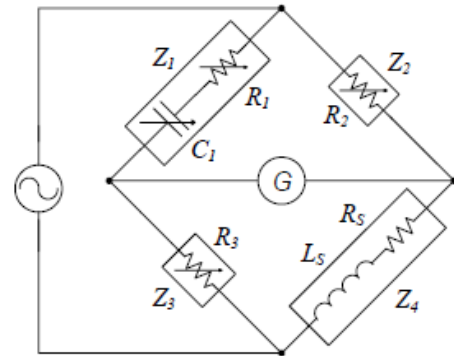
To find the series resistance and inductance, we use the above equations as:



$$L_s = \frac{C_1 R_2 R_3}{1 + \omega^2 R_1^2 C_1^2} = \frac{0.1\text{n} \times 10\text{k} \times 1\text{k}}{1 + (3000)^2 (20\text{k})^2 (0.1\text{n})^2} = 1\text{mH}$$

$$R_s = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{1 + \omega^2 R_1^2 C_1^2} = \frac{(3000)^2 (0.1\text{n})^2 \times 20\text{k} \times 10\text{k} \times 1\text{k}}{1 + (3000)^2 (20\text{k})^2 (0.1\text{n})^2} = 0.018\Omega$$

Schering Bridge

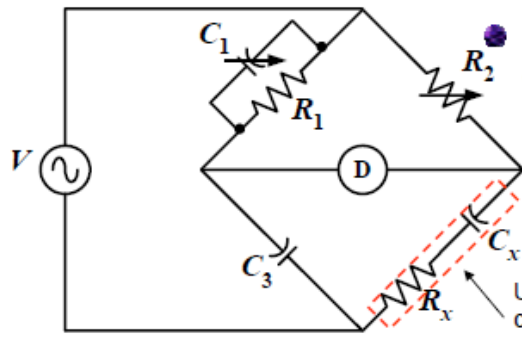

● Used extensively for the measurement of capacitance and the quality of capacitor in term of D

At balance point: $Z_x = Z_2 Z_3 Y_1$

where $Z_2 = R_2$; $Z_3 = \frac{1}{j\omega C_3}$; and $Y_1 = \frac{1}{R_1} + j\omega C_1$

$$R_x - \frac{j}{\omega C_x} = R_2 \left(\frac{-j}{\omega C_3} \right) \left(\frac{1}{R_1} + j\omega C_1 \right)$$

Diagram of Schering Bridge

which expands to $R_x - \frac{j}{\omega C_x} = \frac{R_2 C_1}{C_3} - \frac{j R_2}{\omega C_3 R_1}$

Separation of the real and imaginary terms yields:

$$R_x = R_2 \frac{C_1}{C_3}$$

and

$$C_x = C_3 \frac{R_1}{R_2}$$

Dissipation factor of a series RC circuit: $D = \frac{R_x}{X_x} = \omega R_x C_x$


Dissipation factor tells us about the quality of a capacitor, how close the phase angle of the capacitor is to the ideal value of 90°

For Schering Bridge:

$$D = \omega R_x C_x = \omega R_1 C_1$$

For Schering Bridge, R_1 is a fixed value, the dial of C_1 can be calibrated directly in D at one particular frequency

Wien Bridge

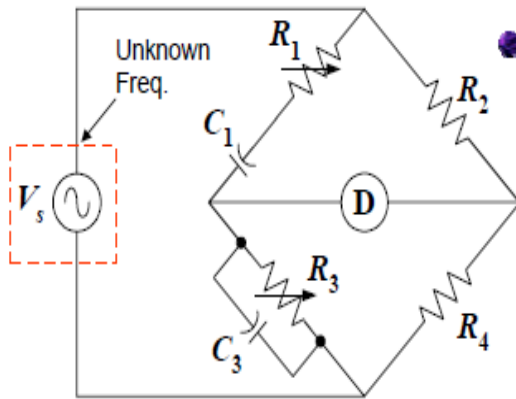

- Measure frequency of the voltage source using series RC in one arm and parallel RC in the adjoining arm

At balance point: $Z_2 = Z_1 Z_4 Y_3$

$$Z_1 = R_1 + \frac{1}{j\omega C_1}; Z_2 = R_2; Y_3 = \frac{1}{R_3} + j\omega C_3; \text{ and } Z_4 = R_4$$

$$R_2 = \left(R_1 - \frac{j}{\omega C_1} \right) R_4 \left(\frac{1}{R_3} + j\omega C_3 \right)$$

Diagram of Wien Bridge

which expands to $R_2 = \frac{R_1 R_4}{R_3} + j\omega C_3 R_1 R_4 - \frac{jR_4}{\omega C_1 R_3} + \frac{R_4 C_3}{C_1}$

$$\begin{cases} \frac{R_2}{R_4} = \frac{R_1}{R_3} + \frac{C_3}{C_1} & \dots\dots\dots (1) \\ \omega C_3 R_1 = \frac{1}{\omega C_1 R_3} & \dots\dots\dots (2) \end{cases}$$

Rearrange Eq. (2) gives $f = \frac{1}{2\pi\sqrt{C_1 C_3 R_1 R_3}}$

In most, Wien Bridge, $R_1 = R_3$ and $C_1 = C_3$

(1) → $R_2 = 2R_4$ (2) → $f = \frac{1}{2\pi RC}$