


## Voltage Follower or Buffer

**What is a Voltage Follower?**

- ❑ A voltage follower is also known as a buffer amplifier, unity gain amplifier, or isolation amplifier**
- ❑ Is an Op-Amp circuit whose output voltage is equal to the input voltage , so the output voltage follows the input voltage ( $V_{out}=V_{in}$ )**
- ❑ A voltage follower Op Amp does not amplify the input signal and has a voltage gain of 1**
- ❑ Gain with feedback or closed loop gain of this circuit is 1**
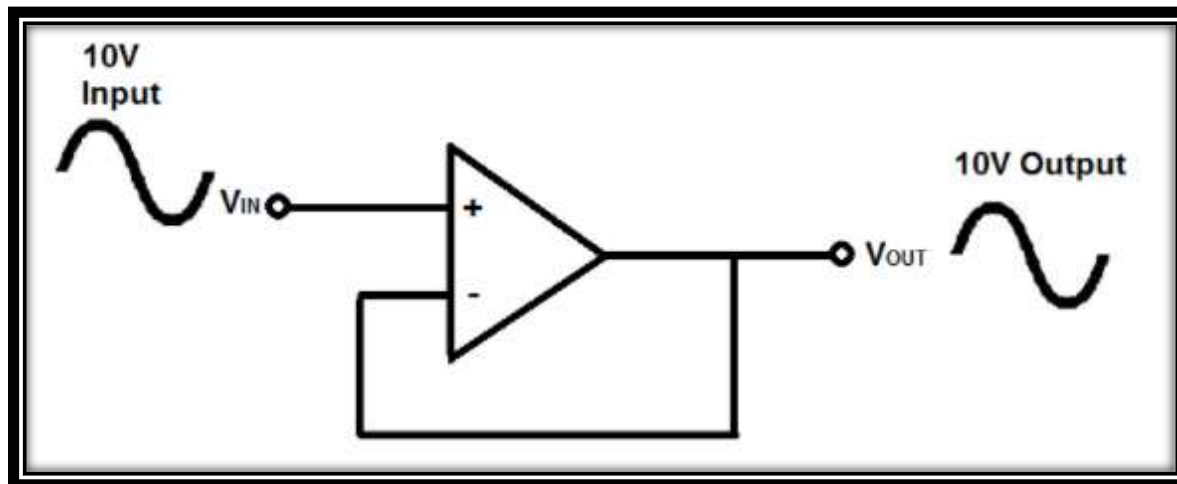
# Part1: Voltage Follower or Buffer

- ❑ The voltage follower provides no attenuation or amplification- only buffering
- ❑ It is a special case of non-inverting Op-Amp, therefore, in this circuit the output signal is in phase with the input signal
- ❑ The feedback resistance  $R_f = 0$  and the input resistance  $R_i = \infty$



# Part1: Voltage Follower or Buffer

## Advantages of Voltage Followers:


- 1) Provides power gain and current gain (voltage gain  $A_v = 1$ )
- 2) Low output impedance to the circuit, which uses the output of the voltage follower
- 3) High input impedance, Op-Amp takes no current from the input
- 4) Loading effects can be avoided
- 5) Isolator purpose, to isolate one circuits to another circuit
- 6) Impedance matching

# Part1: Voltage Follower or Buffer

## **Applications of Voltage Followers:**


- 1) Buffers for logic circuits**
- 2) Sample and hold circuits**
- 3) Active filters, voltage followers can be used to isolate filter stages from each other, when building multistage filters**
- 4) Bridge circuit via a transducer**

# Part1: Voltage Follower or Buffer

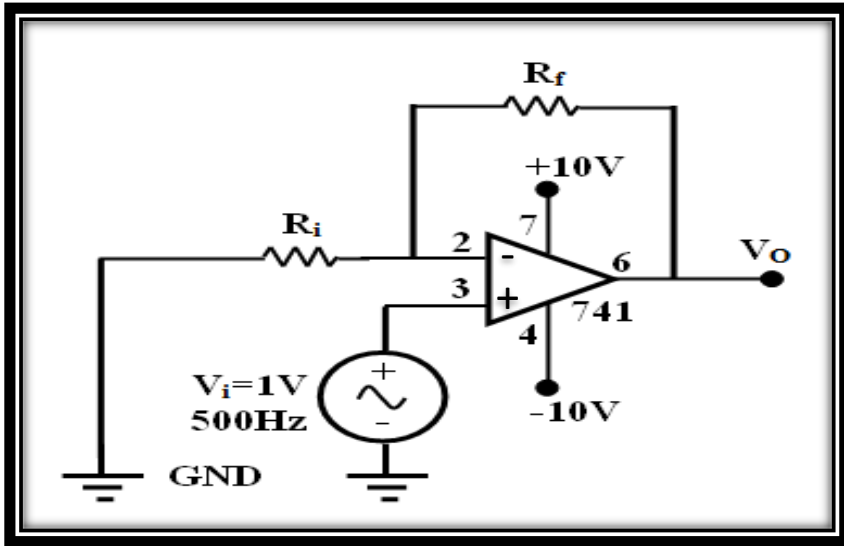

Non-Inverting Circuit
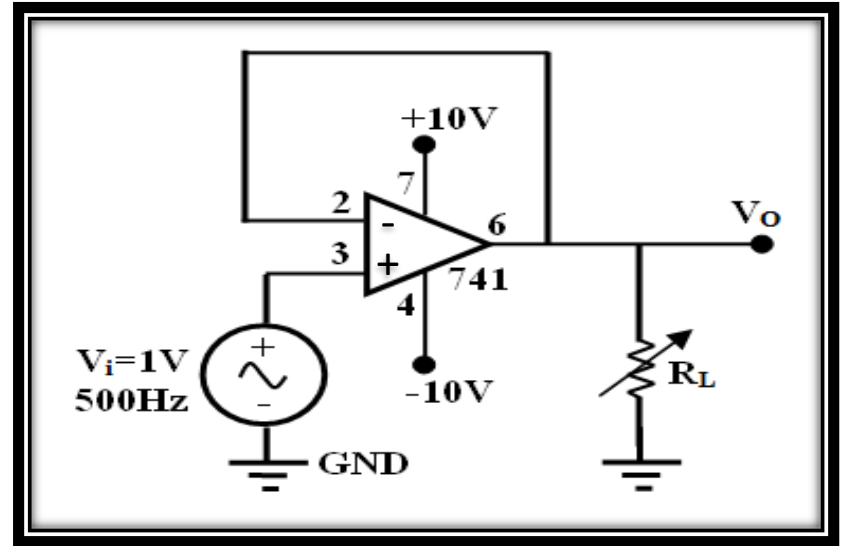
$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$
$$V_o = A_v V_i$$



Voltage Follower (Buffer) Circuit

$$A_v = \frac{V_o}{V_i} = 1 + \frac{0}{\infty} = 1$$
$$R_f = 0, R_i = \infty$$
$$V_o = V_i$$

# Part1: Voltage Follower or Buffer

**The input impedance** of the op-amp is **very high** when a voltage follower or unity gain configuration is used. Sometimes the input impedance is **much higher than 1 Megohm**. So, due to high input impedance, we can apply **weak signals** across the input and **no current** will flow in the input pin from the signal source to amplifier. On the other hand, the **output impedance** is **very low**, and it will produce the **same signal input**, in the output.

**Voltage follower** circuit is used to **create isolation** between two different kind of circuits. Due to high input impedance,, so the **input current is much lower than the output current** while the output voltage follows the input voltage. So the voltage follower provides **large power gain** across its output. Due to this behavior, Voltage follower used as a buffer circuit and can be used to isolate stages while building multistage filters or some other multistage circuit.

# Part2: Integrator Op Amp Circuit

- An **integrator** is an electronic circuit that produces an output that is the integration of the applied input. This section discusses about the **op-amp based integrator**.
- An op-amp based integrator produces an output, which is an integral of the input voltage **applied to its inverting terminal**.
- It is a circuit designed with Op-Amp in such a way that it performs the **mathematical Integration operation**
- its **output** is proportional to the **amplitude** and **time duration** of the **input** applied.
- The integrator circuit layout is same as a **inverting amplifier** but the **feedback resistor** is replaced by a **capacitor** which make the circuit **frequency dependent**.

## Part2: Integrator Op Amp Circuit

- In this case the circuit is derived by the **time duration** of input applied which results in the **charging** and **discharging** of the **capacitor**.
- Initially when the voltage is applied to integrator the **uncharged capacitor** allows **maximum current to pass through it** and no current flows through the Op-Amp due to the presence of virtual ground,
- the capacitor starts to **charge** at the **rate of RC time constant** and its impedance starts to increase with time and a potential difference is develops across the capacitor resulting in charging current to decrease.
- This results in the ratio of capacitor's impedance and input resistance increasing causing a linearly increasing ramp output voltage that continues to increase until the capacitor becomes fully charged.



# Part2: Integrator Op Amp Circuit

Since, the Output voltage is the potential difference across capacitor.

$$V_C = \frac{Q}{C}, \quad Q = CV, \quad I_f = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$$I_i = I_f$$


$$I_i = \frac{V_{in} - V_x}{R_{in}} = C \frac{d(V_x - V_{out})}{dt}$$

$$V^+ = V^- = V_x = 0$$

$$\frac{V_{in}}{R_{in}} = -C \frac{dV_{out}}{dt}$$

$$dV_{out} = -\frac{1}{R_{in}C} V_{in} dt$$
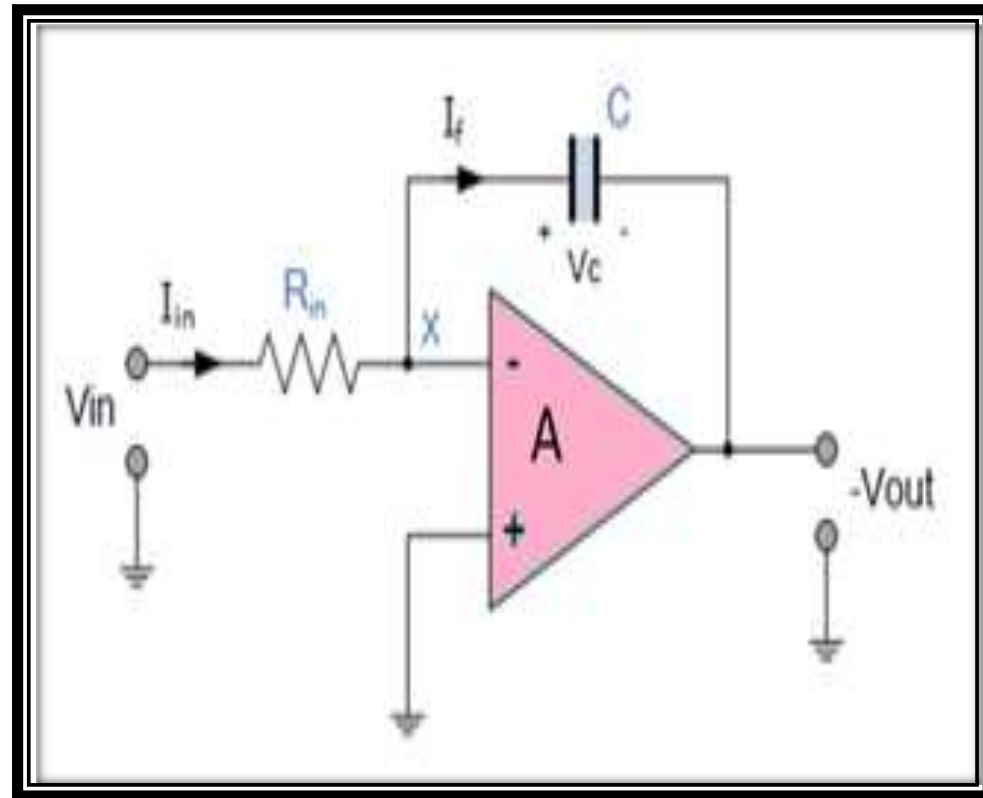
$$V_{out} = -\frac{1}{R_{in}C} \int V_{in} dt$$



$$V_o = -\frac{1}{RC} \int V_i dt$$

# Part3: Differentiator Op Amp Circuit

- A **differentiator** is an electronic circuit that produces an output equal to the **first derivative of its input**. This section discusses about the **op-amp based differentiator** in detail.
- An op-amp based differentiator produces an output, which is equal to the differential of input voltage that is applied to its **inverting terminal**.
- In the differentiator circuit **the input** is connected to the **inverting** output of the Op-Amp through a **capacitor(C)** and a **negative feedback** is provided to the **inverting input** terminal through a **resistor( $R_f$ )**
- which is **same as an integrator circuit** with feedback capacitor and input resistor being **replaced with each other**.
- Here the circuit **performs a mathematical differentiation operation**, and the **output is the first derivative** of the input signal, **180'** out of phase and **amplified** with a **factor  $R_f * C$** .

# Part3: Differentiator Op Amp Circuit

- The capacitor on the input allows only the AC component and restricts the DC, at low frequency the reactance of capacitor is very high causing a low gain and high frequency vice versa but at high frequency the circuit becomes unstable.

# Part3: Differentiator Op Amp Circuit

$$V_C = \frac{Q}{C}, \quad Q = CV,$$

$$I_i = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$$I_i = I_f$$


$$I_i = C \frac{d(V_{in} - V_x)}{dt} = \frac{V_x - V_{out}}{R_f}$$

$$V^+ = V^- = V_x = 0$$

$$C \frac{dV_{in}}{dt} = - \frac{V_{out}}{R_f}$$

$$V_{out} = -R_f C \frac{dV_{in}}{dt}$$

$$V_{out} = -R C \frac{dV_{in}}{dt}$$

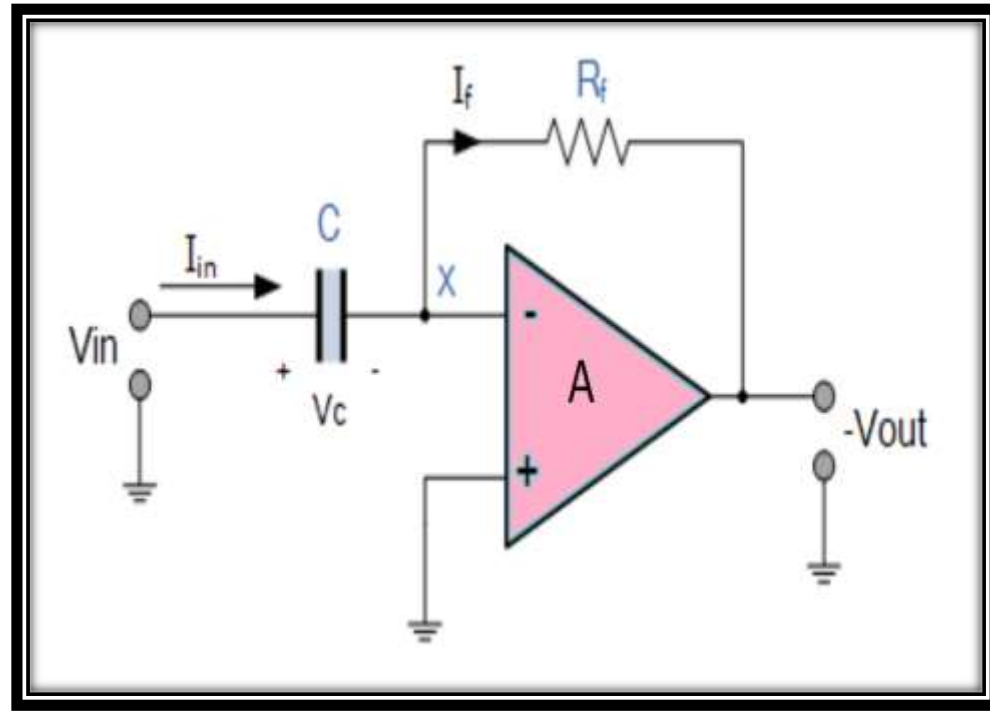

$$V_{out} = -R C \frac{dV_{in}}{dt}$$

**Example:** A 5mV, 1-kHz sinusoidal signal is applied to the input of an OP-AMP integrator, for which  $R = 100 \text{ K}$  and  $C = 1 \text{ } \mu\text{F}$ . Find the output voltage.

**Solution:**

$$-\frac{1}{CR} = \frac{1}{10^5 \times 10^{-6}} = -10$$

The equation for the sinusoidal voltage is

$$v_1 = 5 \sin 2 \pi f t = 5 \sin 2000 \pi t$$

Obviously, it has been assumed that at  $t = 0$ ,  $v_1 = 0$

$$\begin{aligned} v_o(t) &= -10 \int_0^t 5 \sin 2000 \pi t = -50 \left| \frac{-\cos 2000 \pi t}{2000} \right|_0^t \\ &= -\frac{1}{40 \pi} (\cos 2000 \pi t - 1) \end{aligned}$$

**Example:** The input to the differentiator circuit is a sinusoidal voltage of peak value of 5 mV and frequency 1 kHz. Find out the output if  $R = 1000 \text{ K}\Omega$  and  $C = 1 \text{ } \mu\text{F}$ .

**Solution:**

The equation of the input voltage is

$$v_1 = 5 \sin 2 \pi \times 1000 t = 5 \sin 2000 \pi t \text{ mV}$$

$$\text{scale factor} = CR = 10^{-6} \times 10^5 = 0.1$$

$$\begin{aligned} v_o &= 0.1 \frac{d}{dt} (5 \sin 2000 \pi t) = 0.1 \times 5 \times (\cos 2000 \pi t) \times 2000 \pi \\ &= 1000 \pi (\cos 2000 \pi t) \text{ mV} \end{aligned}$$