
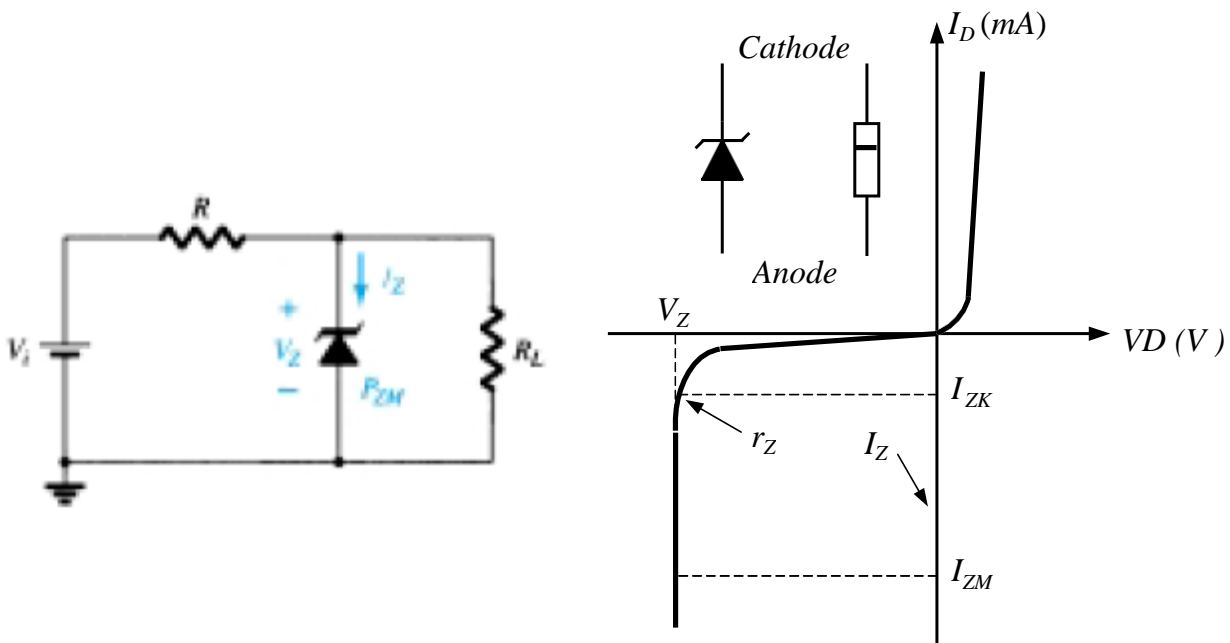
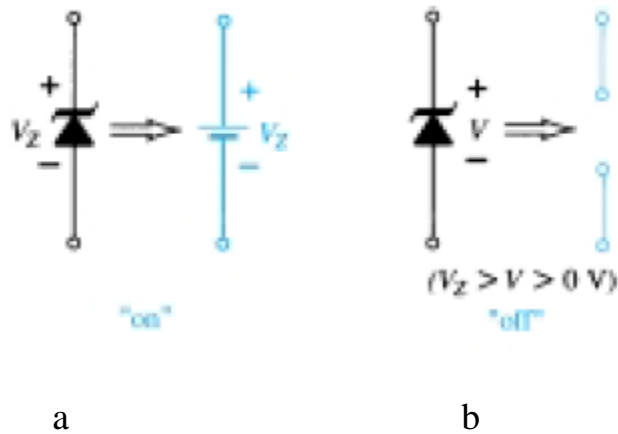

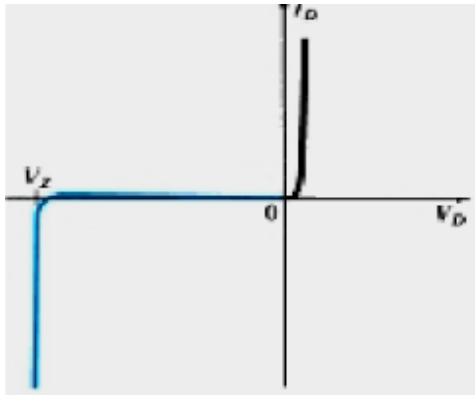
## Zener diode

The analysis of networks employing Zener diodes is quite similar to that applied to the analysis of semiconductor diodes in previous sections. the state of the diode must be determined followed by a substitution of the appropriate model the Zener model to be employed for the “on” state will support a current in the symbol can be as shown in Fig. a. For the “off” state as defined by a voltage less than  $V_Z$  but greater than 0 V with the polarity indicated in Fig. b, the Zener equivalent is the open circuit that appears in the figure below.



For zener diode in an electrical network there operation modes are:

**(a) Fixed  $V_i$ , Variable  $R_L$**


Due to the offset voltage  $V_Z$ , there is a specific range of resistor values (and therefore load current) which will ensure that the Zener is in the “on” state. Too small a load resistance  $R_L$  will result in a voltage  $V_L$  across the load resistor less than  $V_Z$ , and the Zener device will be in the “off” state.

To determine the minimum load resistance of Fig. below that will turn the Zener diode on, simply calculate the value of  $R_L$  that will result in a load voltage  $V_L = V_Z$ .

$$V = V_L = \frac{R_L V_i}{R + R_L}$$

$$R_{Lmin} = \frac{V_Z R}{V_i - V_Z}$$
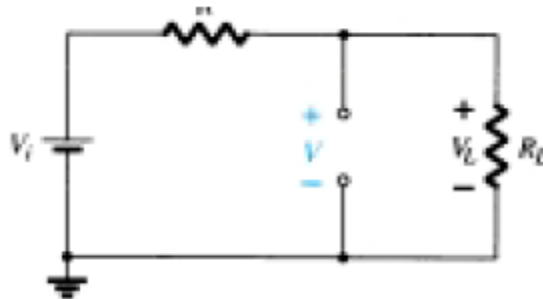
$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$



Resulting in a minimum  $I_Z$  when  $I_L$  is a maximum and a maximum  $I_Z$  when  $I_L$  is a minimum value since  $I_R$  is constant.


Since  $I_Z$  is limited to  $I_{ZM}$  as provided on the data sheet, it does affect the range of  $R_L$  and therefore  $I_L$ . Substituting  $I_{ZM}$  for  $I_Z$  establishes the minimum  $I_L$  as

$$I_Z = I_R - I_L$$

$$I_{Lmin} = I_R - I_{ZM}$$


$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

$$I_{ZM} = \frac{P_{Z(max)}}{V_Z}$$

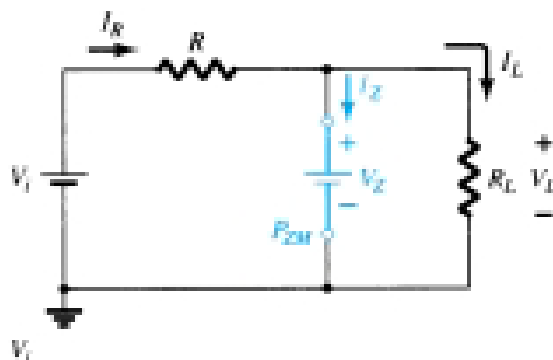

**EXAMPLE:**

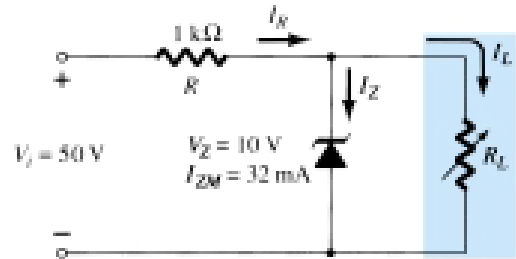- (a) For the network of Figure below, determine the range of  $R_L$  and  $I_L$  that will result in  $V_{RL}$  being maintained at 10 V.  
(b) Determine the maximum wattage rating of the diode.



**Solution**

- (a) To determine the value of  $R_L$  that will turn the Zener diode on, apply

$$R_{L_{\min}} = \frac{RV_Z}{V_i - V_Z} = \frac{(1\text{ k}\Omega)(10\text{ V})}{50\text{ V} - 10\text{ V}} = \frac{10\text{ k}\Omega}{40} = 250\ \Omega$$

The voltage across the resistor  $R$  is then determined by

$$V_R = V_i - V_Z = 50\text{ V} - 10\text{ V} = 40\text{ V}$$

And


$$I_R = \frac{V_R}{R} = \frac{40\text{ V}}{1\text{ k}\Omega} = 40\text{ mA}$$

then  $I_{L_{\max}} = 40\text{ mA}$ , The minimum level of  $I_L$  is then determined


$$I_{L_{\min}} = I_R - I_{ZM} = 40\text{ mA} - 32\text{ mA} = 8\text{ mA}$$

$$R_{L_{\max}} = \frac{V_Z}{I_{L_{\min}}} = \frac{10\text{ V}}{8\text{ mA}} = 1.25\text{ k}\Omega$$

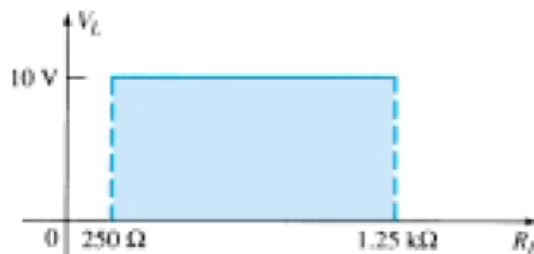A plot of  $V_L$  versus  $R_L$  appears in Fig.



(a)

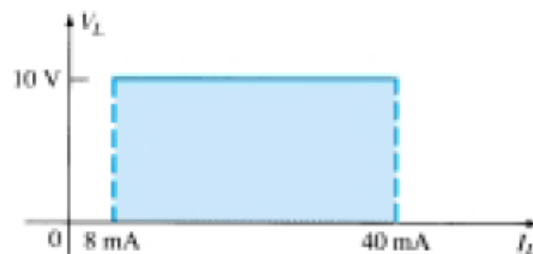

(b)

- (b)


$$\begin{aligned} P_{\max} &= V_Z I_{ZM} \\ &= (10\text{ V})(32\text{ mA}) = 320\text{ mW} \end{aligned}$$

**(b) Fixed  $R_L$ , Variable  $V_i$**

For fixed values of  $R_L$  in Fig. below, the voltage  $V_i$  must be sufficiently large to turn the Zener diode on. The minimum turn-on voltage  $V_i = V_{i\min}$  is determined by

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

$$V_{i\min} = \frac{(R_L + R)V_Z}{R_L}$$

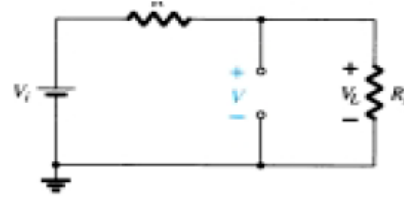


$V_i$  is limited by the maximum Zener current. The maximum value of  $I_{ZM}$ . Since


$$I_{R_{\max}} = I_{ZM} + I_L$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z$$

$$I_{ZM} = \frac{P_{Z(\max)}}{V_Z}$$

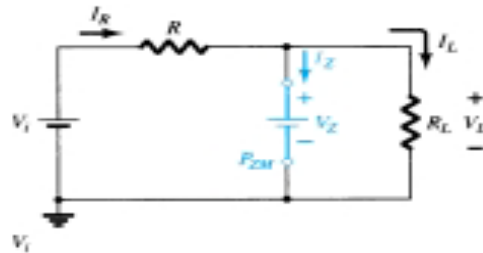

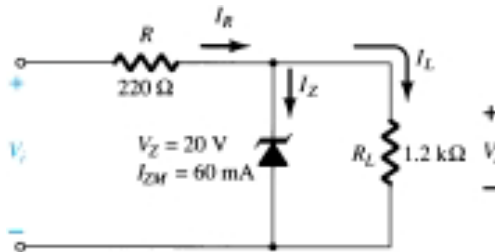EXAMPLE: Determine the range of values of  $V_i$  that will maintain the Zener diode of Figure below in the “on” state.



Solution

$$V_{i\min} = \frac{(R_L + R)V_Z}{R_L} = \frac{(1200 \Omega + 220 \Omega)(20 \text{ V})}{1200 \Omega} = 23.67 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20 \text{ V}}{1.2 \text{ k}\Omega} = 16.67 \text{ mA}$$

$$I_{R_{\max}} = I_{ZM} + I_L = 60 \text{ mA} + 16.67 \text{ mA}$$


$$= 76.67 \text{ mA}$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z$$

$$= (76.67 \text{ mA})(0.22 \text{ k}\Omega) + 20 \text{ V}$$

$$= 16.87 \text{ V} + 20 \text{ V}$$

$$= 36.87 \text{ V}$$

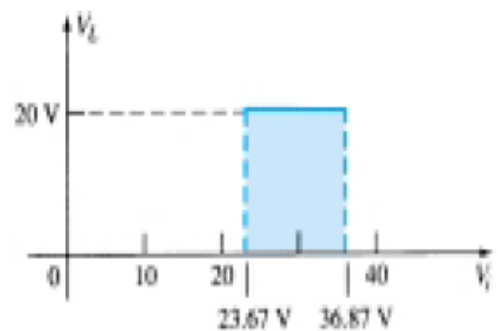

A plot of  $V_L$  versus  $V_i$  is provided in Fig.