

2- D.C Voltmeter:

A voltmeter is always connected in parallel with the element being measured and measures the voltage between the points across which it's connected. Most d.c voltmeters employ a PMMC meter with a series resistor as shown. The series resistance should be much larger than the impedance of the circuit being measured, and they are usually much larger than R_m .

$$R_s = R_T - R_m$$


$$R_s = \frac{V_{range}}{I_m} - R_m$$

$$I_m = I_{FSD}$$

The ohm/volt sensitivity of a voltmeter is given by:

$$S_v = \frac{R_m}{V_{FSD}} = \frac{1}{I_{FSD}} = \frac{\Omega}{V} \text{ rating}$$
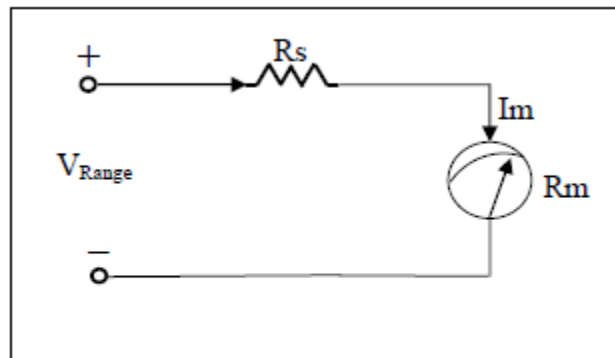
$$S_{Range} = \frac{R_m + R_s}{V_{Range}} = \frac{1}{I_{Range}} = \frac{\Omega}{V}$$



So the internal resistance of the voltmeter or the input resistance of the voltmeter is

$$R_v = V_{FSD} \times \text{sensitivity}$$

Example:

We have a micro ammeter and we wish to adapt it to measure 1 volt full scale, the meter has an internal resistance of 100Ω and I_{FSD} of $100\mu A$.

Sol:-

$$R_s = \frac{V}{I_m} - R_m$$

$$R_s = \frac{1}{0.0001} - 100 = 9900\Omega = 9.9K\Omega$$

So we connect with **PMMC meter** a series resistance of $9.9K\Omega$ to convert it to a voltmeter


Extension of Voltmeter Range:

The voltage range of d.c voltmeter can be further extended by a number of series resistance selected by a range switch; such a voltmeter is called a multirange voltmeter.

a) *Direct D.c Voltmeter Method:*

In this method, each series resistance of multirange voltmeter is connected indirect with PMMC meter to give the desired range.

$$R_{s*} = \frac{V_*}{I_m} - R_m$$

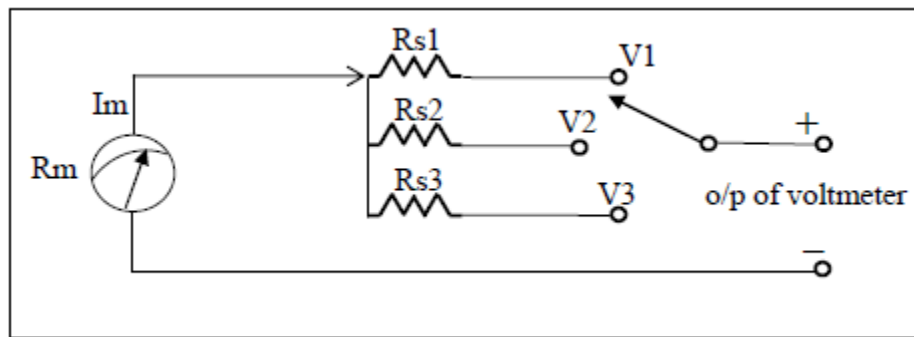
**b) *Indirect D.c Voltmeter Method:***

In this method, one or more series resistances of the multirange voltmeter are connected with PMMC meter to give the desired range.

$$R_{s1} = \frac{V1}{I_m} - R_m$$

$$R_{s2} = \frac{V2 - V1}{I_m}$$

$$R_{s3} = \frac{V3 - V2}{I_m}$$

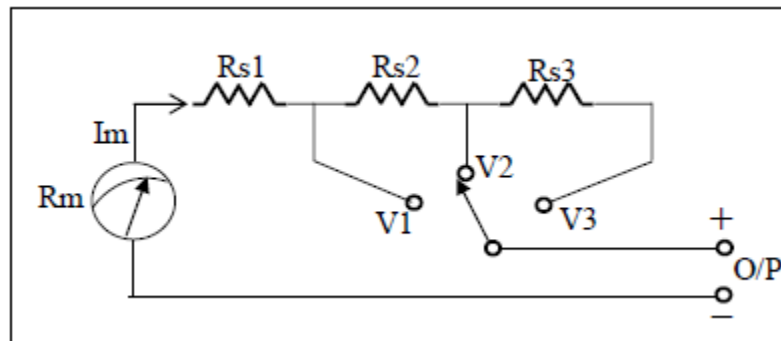

Example (1):

A basic d'Arsonval movement with an internal resistance of 100Ω and half-scale current deflection of 0.5 mA is to be converted by indirect method into a multirange d.c voltmeter with voltages ranges of 10V , 50V , 250V , and 500V .

Sol:

$$I_{\text{FSD}} = I_{\text{HSD}} \times 2$$

$$I_{\text{FSD}} = 0.5\text{mA} \times 2 = 1\text{mA}$$

$$R_{s1} = \frac{V1}{I_m} - R_m$$


$$R_{s1} = \frac{10}{1\text{mA}} - 100 = 9.9\text{K}\Omega$$

$$R_{s2} = \frac{V2 - V1}{I_m}$$

$$R_{s2} = \frac{50 - 10}{1 \times 10^{-3}} = 40\text{K}\Omega$$

$$R_{s3} = \frac{250 - 50}{1 \times 10^{-3}} = 200\text{K}\Omega$$
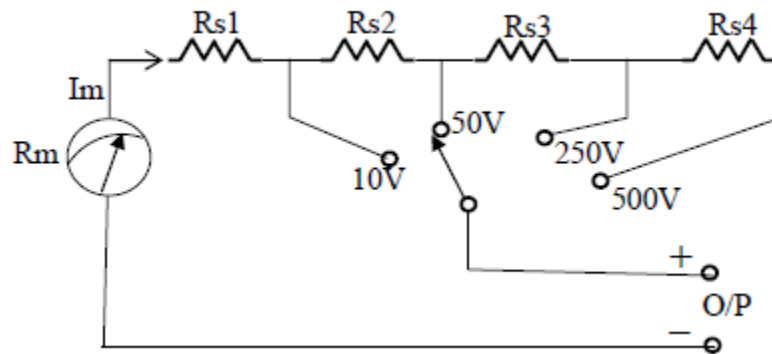
$$R_{s4} = \frac{500 - 250}{1 \times 10^{-3}} = 250\text{K}\Omega$$



Example (2):

Design d.c voltmeter by using direct method with d'Arsonval meter of 100Ω and full-scale deflection of $100\mu\text{A}$ to give the following ranges: 10mV , 1V , and 100V .

Sol:

$$R_{s*} = \frac{V_*}{I_m} - R_m$$

$$R_{s1} = \frac{V1}{I_m} - R_m$$

$$R_{s1} = \frac{10\text{mV}}{100\mu\text{A}} - 100 = 0\Omega$$

$$R_{s2} = \frac{1}{100 \times 10^{-6}} - 100 = 9.9\text{K}\Omega$$

$$R_{s3} = \frac{100}{100 \times 10^{-6}} - 100 = 99.9\text{K}\Omega$$

